

The *SPECTRUM* SYNTHESISER

Professional
Quality
Monophonic
Instrument

- ★ Low Cost
- ★ Easy to Construct
- ★ FM and Sync.
- ★ Stereo Outputs
- ★ Sequencer Effects
- ★ Interface Facilities
- ★ Four Octave Keyboard
- ★ Performance Controller



Since publication of the Spectrum articles was delayed earlier this year, many improvements have been made to the original design. The synthesiser can still be built for around £200, plus cabinet, yet offers features found only on expensive commercial instruments.

For the benefit of newcomers to the magazine, and to bring our regular readers up to date with the improvements that have been made, we will be


reprinting some of the original material. The project will be published in two parts, containing sufficient information to enable experienced constructors to build the Spectrum. PCB track layouts and component overlays, cabinet drawings, a wiring chart and more comprehensive circuit descriptions are available in the Spectrum Synthesiser book, available from Maplin Publications for £1 plus 24p postage.

The Spectrum is a monophonic two oscillator switch-linked synthesiser featuring advanced specification, constructional simplicity and low cost. Modulation, timbre control, and interface facilities not found on any comparable synthesiser make it extremely powerful and versatile for keyboard playing, sound effects and many other home, stage, or studio applications. Construction is simplified by the use of integrated circuits that each perform major synthesiser func-

tions with few external components. No gluing of contact blocks or bending of gold wires is needed to assemble the keyboard contacts; a new contact system only requires soldering of the contacts and drilling of the chassis to mount the contact PCB.

Figure 1 shows a block diagram of the synthesiser and the front panel legending is reproduced below. Modulation routing is accomplished by source and function switches and depth controls, rather than the usual

method of providing each source with its own depth for each controlled function found on some small synthesisers. Switching is most suitable for a large number of sources as here, and allows fast selection of source and selection of modulation effects with preset depths, in favour of simultaneous modulation of one parameter by more than two signals. Six modulation signals are available: keyboard, controller, low frequency oscillator (LFO), envelope generator, noise generator

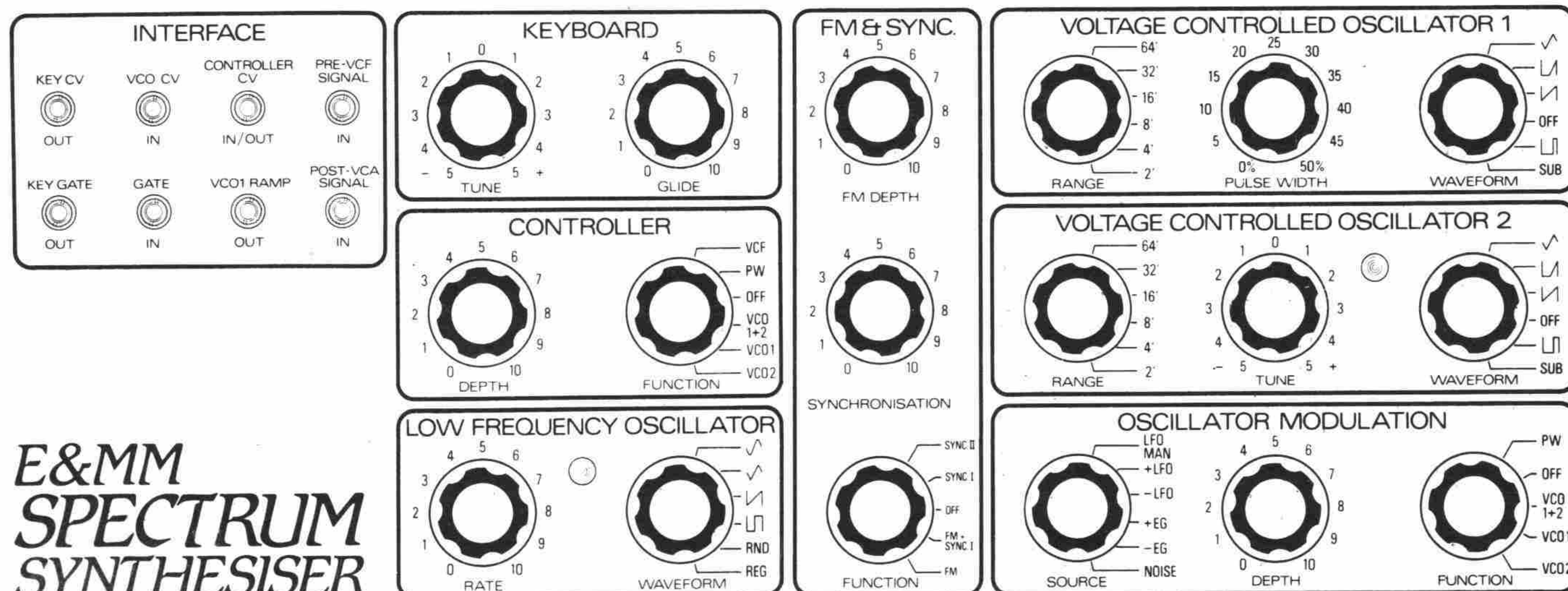

E&MM
SPECTRUM
SYNTHESISER

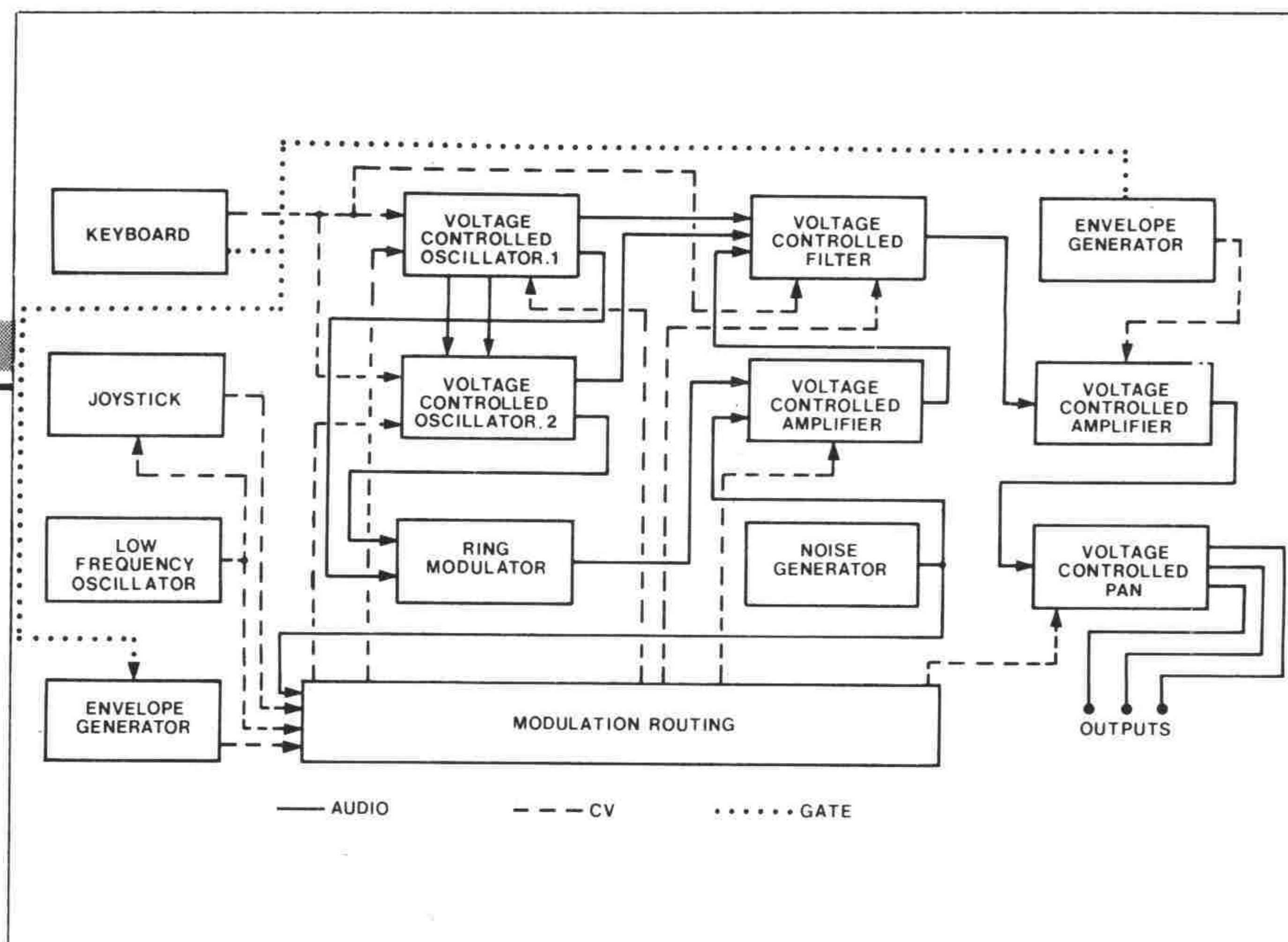


Figure 1. Block diagram of the Spectrum Synthesiser.

and external. The keyboard is of the highest note priority type and has a glide which always completes even after the key is released — this makes the keyboard much more useful as a controller for effects sounds. The joystick controller routes a voltage dependent on the side-to-side position of the stick to various voltage controlled circuits, allowing it to be used to control the pitch (pitch bend) or timbre. The external voltage fed into the controller jack can override or add to the joystick voltage for control by additional synthesiser equipment, or a pedal can be plugged in and used for control by attenuating a fixed joystick voltage.

The low frequency oscillator generates random and regular sample and hold effects in addition to the four common waveforms. The regular S/H option allows rising and falling scales, rising and falling repeating groups of two, three or more notes, and other sequencer-like effects, with the pattern controlled by the LFO rate. A LED displays the LFO cycle and the joystick's vertical position determines the amplitude at the LFO manual output. The envelope generator is of the exponen-

tial ADSR type and, like the LFO, has + and - outputs that can be separately selected for each controlled parameter. The envelope generator shares its gate signal with the envelope shaper, which determines the loudness contour of each note. 'Single' on the gate selector switch causes gating each time a first key is depressed; 'Multiple' retriggers, when any new note is played, allowing fast runs without 'missed' notes. 'Hold' keeps the gate high for continuous effects, and 'LFO' causes gating on each LFO cycle. In the 'Repeat' position the envelope generator retriggers at the end of the decay period, acting as an additional LFO with variable symmetry. This allows complex rhythmic effects when used with the LFO, and gives great scope for 'backdrop' sounds based around complex S/H patterns with periodic timbre sweeping effects derived from the EG. 'Key Repeat' brings in the repeat only when a key is held, allowing key-synchronised repeating notes and delayed modulation (the delay determined by the attack time). An LED indicates the EG's attack segment.

The voltage controlled oscillators


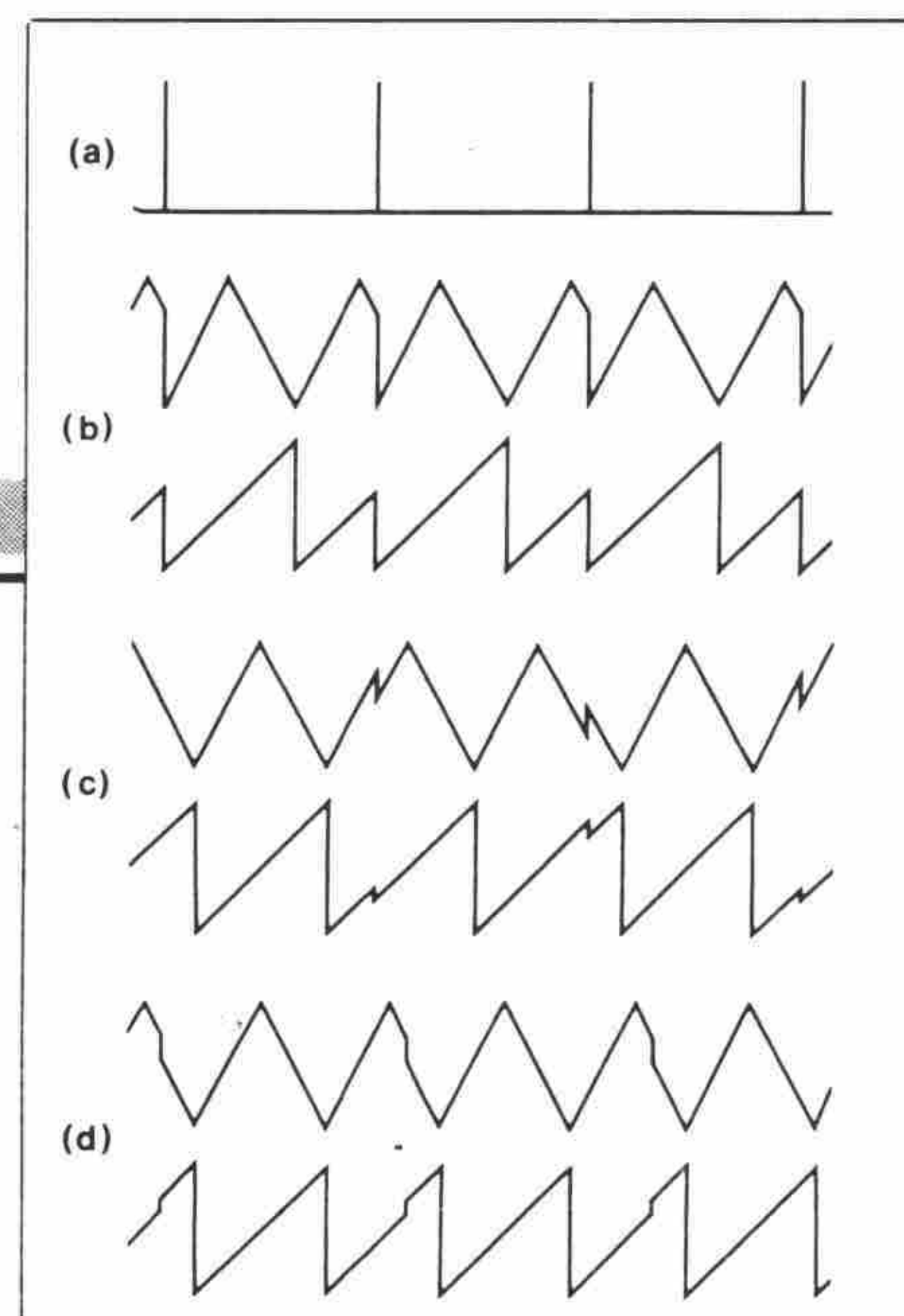


Figure 2. Sync. waveforms. (a) Sync. pulses. (b) Sync. I. (c) Sync. II. (d) Sync. II with decreased VC01 frequency.

(VCOs) each have six switched octave ranges and five waveforms. The sub-octave output is a pulse wave with a square wave added an octave below, making the sound fuller and richer. The tuning LED detects the beats between the oscillators, and indicates when the pitches are in simple musical intervals, useful for tuning without sounding a note (e.g. on stage). The pulse width of VCO 1 is variable, and VCO 2 has a tune control with a \pm one fifth range.

The VCOs can be used together to provide a vast range of sounds not possible with basic synthesisers having only waveform, shape, VCF cutoff and VCF resonance as the controls affecting basic timbre. This is done by frequency modulation and synchronisation — special features of this design. FM uses the triangle output of VCO 1 to modulate the frequency of VCO 2 up to $\pm 100\%$ giving a whole range of non-harmonic tones for bell, gong and chime sounds etc. Synchronisation gives various waveforms from VCO 2 (see Figure 2) which have particular bands of harmonics emphasised for strong, voice-box-like sounds. This is achieved by resetting the output of VCO 2 upon each

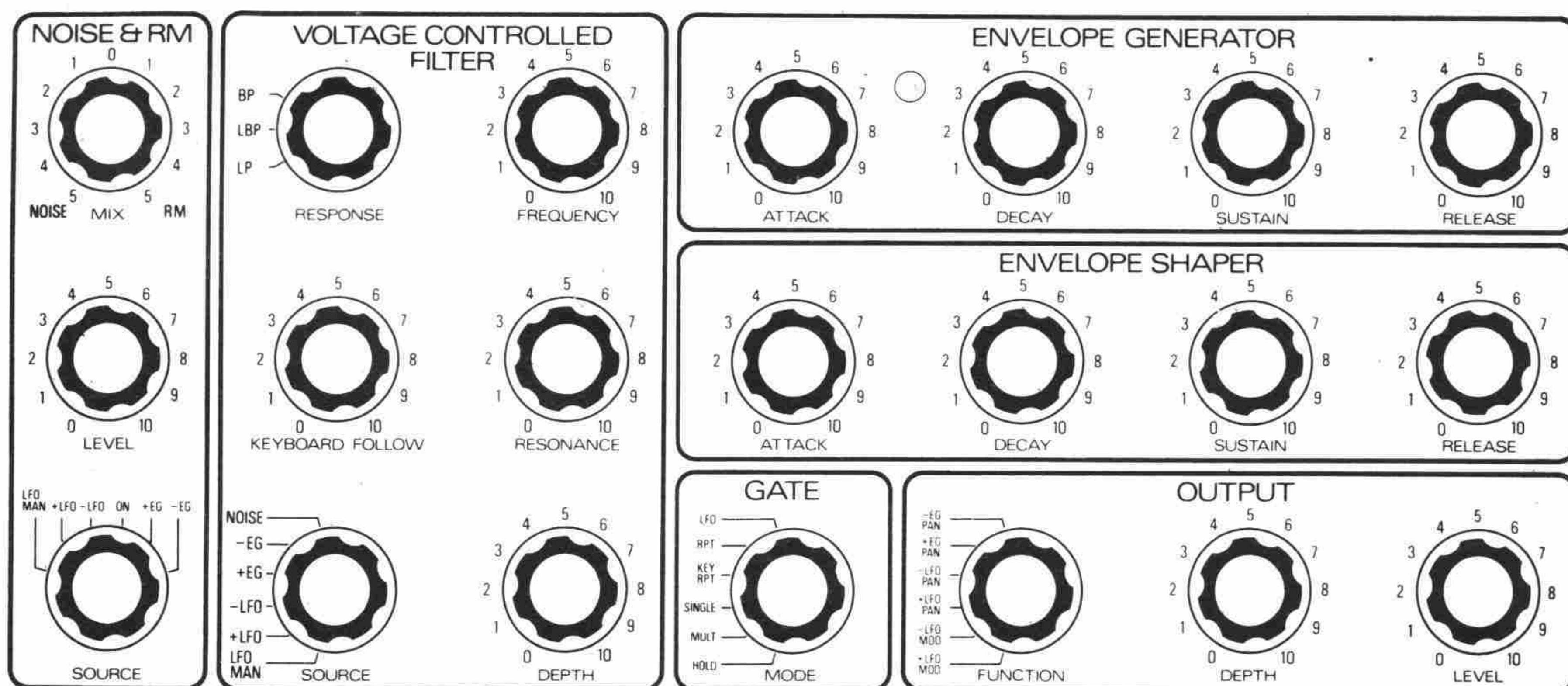

cycle of VCO 1, so the tones generated are always harmonic. Two modes of sync. are provided: Sync. I is that normally found on rampwave oscillators, the VCO 2 waveform beginning in the same way after each reset; Sync. II is something totally new — the triangle output is set to mid way each time but then carries on in the same direction in the new cycle. VCO 2 locks on to VCO 1 harmonics with the change from one harmonic to the next emphasised by a sharp change in tone. This enables automatic arpeggiation and incredible tone sweeps to be obtained since VCO 2 now is effectively a voltage controlled waveform generator/frequency multiplier. The sync. control attenuates the pulses fed to VCO 2 so that it only resets if the wave form is above a certain threshold, resulting in the oscillators being locked together in musical intervals (3rds, 5ths etc). Simultaneous Sync. I and FM produces harmonic tones with the shape of FM-ed waveforms within each cycle.

The ring modulator uses triangle and square VCO waveforms to provide further complex tones. Its output is mixed with the noise signal and fed into a special voltage controlled amplifier (VCA). This can be controlled by the LFO or EG, and gives the signals their own loudness contours. Hence noise 'chiffs' can be added to notes, or ring modulation set to swell in as a note decays.

The VCA output is fed to the voltage controlled filter (VCF) mixed with the VCO outputs. The VCF offers the two most useful responses, low pass and band pass, plus an intermediate response for bright sounds that remain strong in lower harmonics. Cutoff frequency and resonance controls perform their normal functions and a keyboard follow control determines how the cutoff frequency varies over the keyboard range.

After envelope shaping, the signal is fed to the voltage controlled pan circuit which can modulate the location of the sound in the stereo field by the LFO or EG signals. The stereo outputs can also be used for voltage control of the depth

of external effects such as reverb, phase, and echo, by routing one signal via the effects unit and one direct to the amplifier. A mono output is also provided, and the VCA can also be used for additional amplitude modulation with the LFO as source (for tremolo and other effects).

The interface jacks allow connection to external devices such as sequencers, additional VCO banks, waveform processors etc. The Spectrum Synthesiser uses the 1V/octave CV standard, and can be interfaced to any other exponential CV synthesiser.

Keyboard

The moving contacts are silver-plated springs, each fixed at one end and moved at the other by the plunger of the respective key such that the spring makes contact with two palladium bars when the key is depressed (Figure 3). The first bar is connected to the sample and hold circuit which stores the voltage representing the last key depressed, and the second to a circuit which generates a gate signal for the S/H and the envelope generators. The moving contacts connect to the divider chain (see Figure 4). These functions are usually carried out by separate contact pairs, where unless the contacts are precisely set up, note-jumping will occur when the envelope is gated before the S/H receives the new key voltage. The system used here is immune from this since the construction ensures the correct sequence of operation, and no initial setting up is required. The keyboard recommended in the parts list has removable key plungers so that cleaning the contacts is much easier too. Unclipping a plunger allows access to the sides of the bars and springs that meet.

Power Supply Unit

The Power Supply Unit consists of two identical circuits providing the positive and negative supplies, driven by a dual secondary transformer. Each secondary produces about 21V when the AC signal is rectified and smoothed, and is fused for protection in the event

of a power supply fault. Regulation is carried out by the well-known uA723 regulator IC which is used with an external power transistor in series pass mode to provide the required current. This current limits at 270 mA when the voltage across series resistor R1 (R2 in the -ve side) reaches 0.6V. RV1 (RV2) allows the rail voltage to be adjusted to exactly 15V, and D1 (D2) protects against reverse polarity, again in the event of a fault. The + 15V regulated output of the side based around IC2 is connected to 0V of the IC1 side, giving the -15, 0, + 15V supply rails.

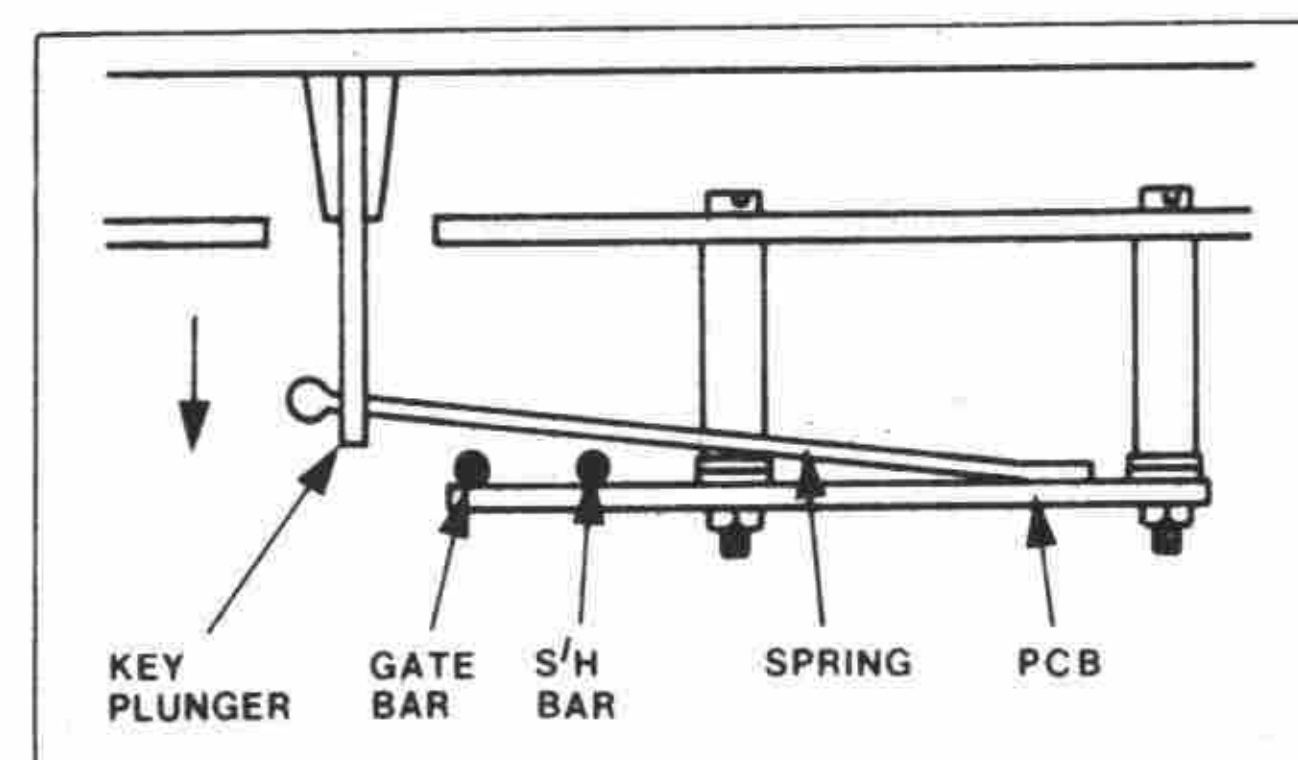


Figure 3. Key contact construction.


Keyboard Controller

Figure 6 shows the circuit diagram of the keyboard controller. Connections 1 and 2 are the bottom and top respectively of the keyboard divider chain. This is arranged in the feedback loop of IC3a, which drives a current of about 1.8mA through the divider chain.

IC3b generates a signal that is used, after processing, to gate the envelope generators and key voltage sample and hold. With no keys depressed, the non-inverting input is held at 0V by R60 and since the inverting input is at +0.83V (determined by R58) IC3b's output is at its negative extreme, almost -15V. When a key is depressed, the voltage at the inverting input rises to between 1.7 and 5.7V since the gate bus-bar is connected to the divider chain by the contact of the depressed key, and the output of IC3b goes high.

TR3 is a FET which acts as a voltage controlled switch in the sample-and-hold circuit around C11. It is normally held off by the negative output voltage of IC3b, via R62 and D14, but upon this going positive it is turned on and C11

Figure 4. Circuit of key contact assembly.

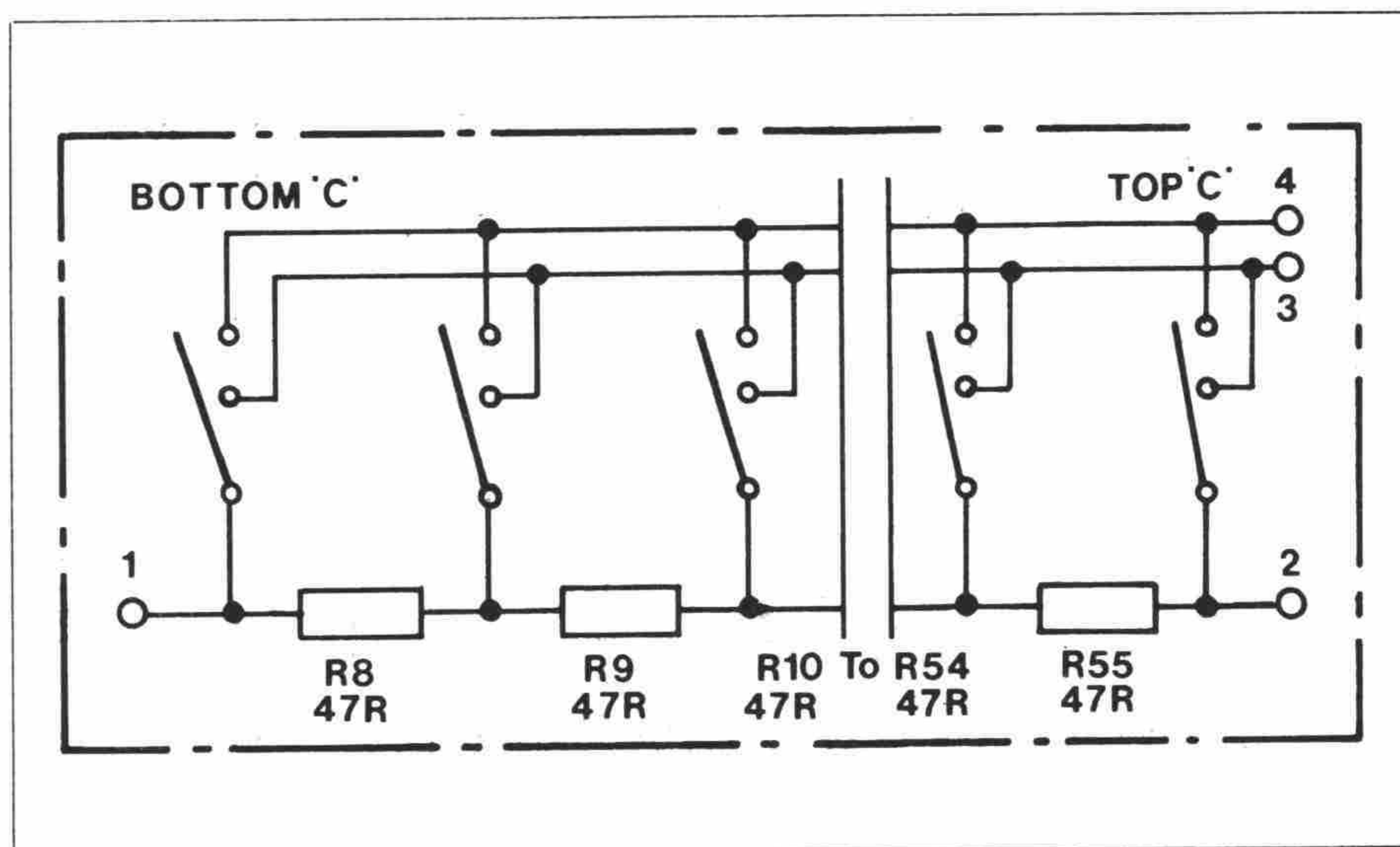

charges to the voltage on the S/H bus-bar (connection point 3). Since the contact spring makes with this before the gate bus-bar, the new key voltage is always ready for sampling by the time the FET is turned on. IC5 is a FET input op-amp with a very low input bias current. This ensures that when the key is released and TR3 turns off the charge on C11 is retained with the minimum of 'droop'. Even when C11 is a high quality type (as it must be), leakage in this component predominates over the input current of IC5a. On the prototype, it took about 15 minutes for middle A to drift up to A#.

If a new note is played on the keyboard before the previous one is released, a new CV is generated, but since the key gate signal remains high, the EGs will not restart their envelopes. This can be a problem when percussive envelopes are used, fast keyboard runs giving missed notes. The problem is eliminated by detecting a change in CV at the sample and hold output, and generating a key retrigger signal for the EGs. IC4a is a high-gain differentiator that produces a pulse for each change in the value of the CV. These pulses are rectified and squared up by the comparator IC4b, and lengthened by D16, R75, and C12 to a minimum of 5mS.

Contact bounce produces a very ragged CV change when a note is depressed while one is already down, and this in turn produces a multiple pulse at the output of IC4b. The circuit around IC6c generates a clean 500uS pulse from this signal — most important for external devices such as sequencers which count in response to triggers from the keyboard.

The de-bounced gate signal from IC6a is inverted by TR5, which drives the 'key gate out' interface jack. D19 causes the gate out signal to go low in response to the key retrigger signal. TR5 is arranged to pull the output to +15V to generate the gate signal — this system allows gates from different sources to be connected together, providing an OR-function that gates the controlled device if any source signal is high.

The output of the sample-and-hold circuit (TR3, C11, IC5a) is passed to the glide circuit (R74, RV4, C13, IC5b) which produces sweeps between successive notes. The time taken for a new note voltage to be reached is controllable from almost instantaneous to five seconds for one octave by RV4. IC5b is a low input bias current op-amp, avoiding any voltage drop across RV4 that would cause a perceptible pitch error with maximum glide.

Low Frequency Oscillator

The Low Frequency Oscillator (LFO) of a synthesiser provides periodic waveforms for the control of other modules to produce modulation of pitch, timbre, amplitude etc. When the synthesiser is being used other than for simple melodic playing, the LFO is often the main control source, and must have a wide frequency range and a choice of precise waveforms. The Spectrum LFO has a range of over 1000:1, from 0.04Hz (25 seconds per cycle) to about 42Hz. Sine, triangle, ramp, and square waveforms are available, plus two additional step-type waveforms, one giving a new

random voltage on each cycle, the other producing a wide range of repeating sequences. A LED flashes to indicate the LFO cycle and is very useful for quickly checking or setting the rate. Particular attention has been paid to waveform precision, and good symmetry is retained over the frequency range. Unlike many other designs, no setting up is required.


Circuit

Figure 8 shows the circuit of the LFO. It is based around IC8, IC9a, TR8, 9, 16 and 17, which form a precision triangle and square wave generator. IC8 is an integrator driven by the voltage at the wiper of RV6, the Rate control.

IC9a is a comparator which reverses the voltage at the integrator input when its output reaches thresholds set by R100 and 101, so the integrator output ramps up and down between fixed levels generating a triangle wave.

The method of producing the ramp-wave is rather unusual. The triangle and square waves are mixed and half-wave rectified by IC9b. Since only positive output values are allowed, the signal is 'cut off' at zero volts when the square wave is high i.e. when the triangle wave is falling. The result is a positive going

Figure 5. Power supply circuit.

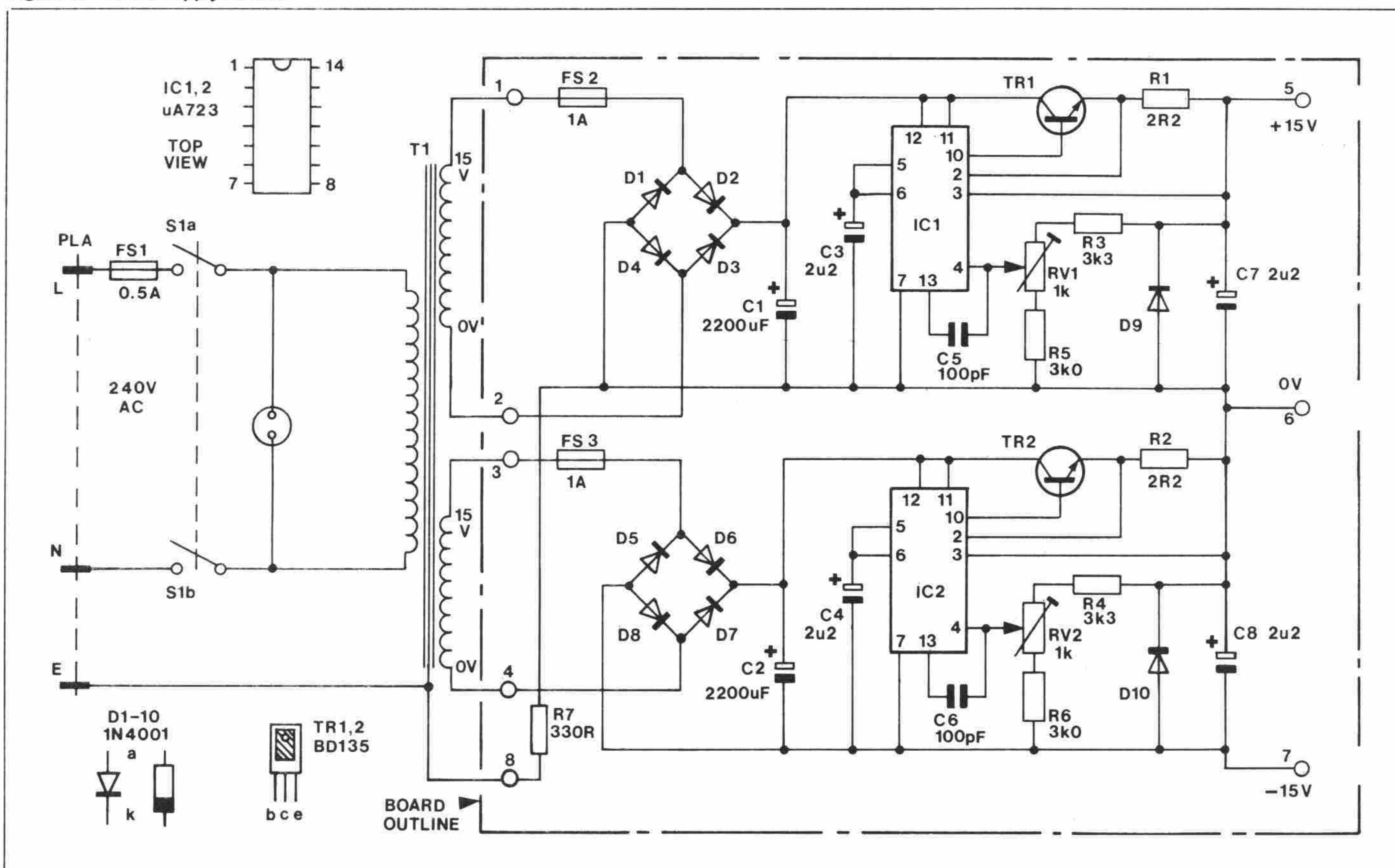

half-wave rectified ramp wave, which gives a complete ramp wave when the triangle wave (and an offset) is added, producing a slope during the 'flat' half cycle and half-cancelling the slope during the other half.


The sine wave is generated by D24-27 and associated resistors. Minimum harmonic content of a sine wave used for control purposes is not as important as smoothness of the waveform — it should have no sharp changes of gradient and should slow down gradually towards the peaks.

The 'LFO MAN' output gives the selected waveform at a level controlled by the joystick y-axis. RV7 is the joystick pot, acting as potential divider fed by

+LFO and buffered by IC12b. Since the joystick needs to move in both directions, there will be an indeterminate amount of LFO signal on the wiper of RV7 when the stick is central. RV8 cancels this signal out by introducing the same polarity signal to the inverting input of IC12b. This means that moving the joystick one way will give an increasing +LFO signal on the LFO MAN output, while the other direction will give -LFO.

The regular and random LFO waveforms are step-type functions which change level abruptly at the beginning of each cycle and remain fixed until the next cycle starts. They are produced by the sample-and-hold circuit around C19 and differ in the type of input to the sample-and-hold (S/H). The random waveform has the output of the noise generator as its source, producing a new random voltage in the range $\pm 2.5V$ every cycle. The regular waveform is more complicated since the source is periodic — a 20Hz rampwave which is synchronised to the main LFO. This is generated by the oscillator around TR6, 7 and C15.

The effect of sampling a constant frequency rampwave at a regular rate is to produce complex repeating sequences of voltages, the sequence length and type being determined by the sampling and sampled frequencies. This is often used to produce note sequences by modulating a VCO with the sample-and-hold output, but suffers from the disadvantage that the slightest change in sampling frequency or the frequency of the sampled waveform changes the effect. In practice it is very difficult to get a precisely repeating sequence, rather than one which has a repetitive 'theme' that steadily changes as a part of a truly repeating sequence with a much longer period. In other words, the results are often too complex and uncontrollable to be useful, and some method is needed to restrict the S/H waveform to shorter repeating sequences. The Spectrum is unique in providing this, and does so by prematurely resetting the rampwave oscillator if it is near the end of its cycle when sampling occurs. Referring back to the LFO circuit diagram, this is achieved by C17 and R99 which couple

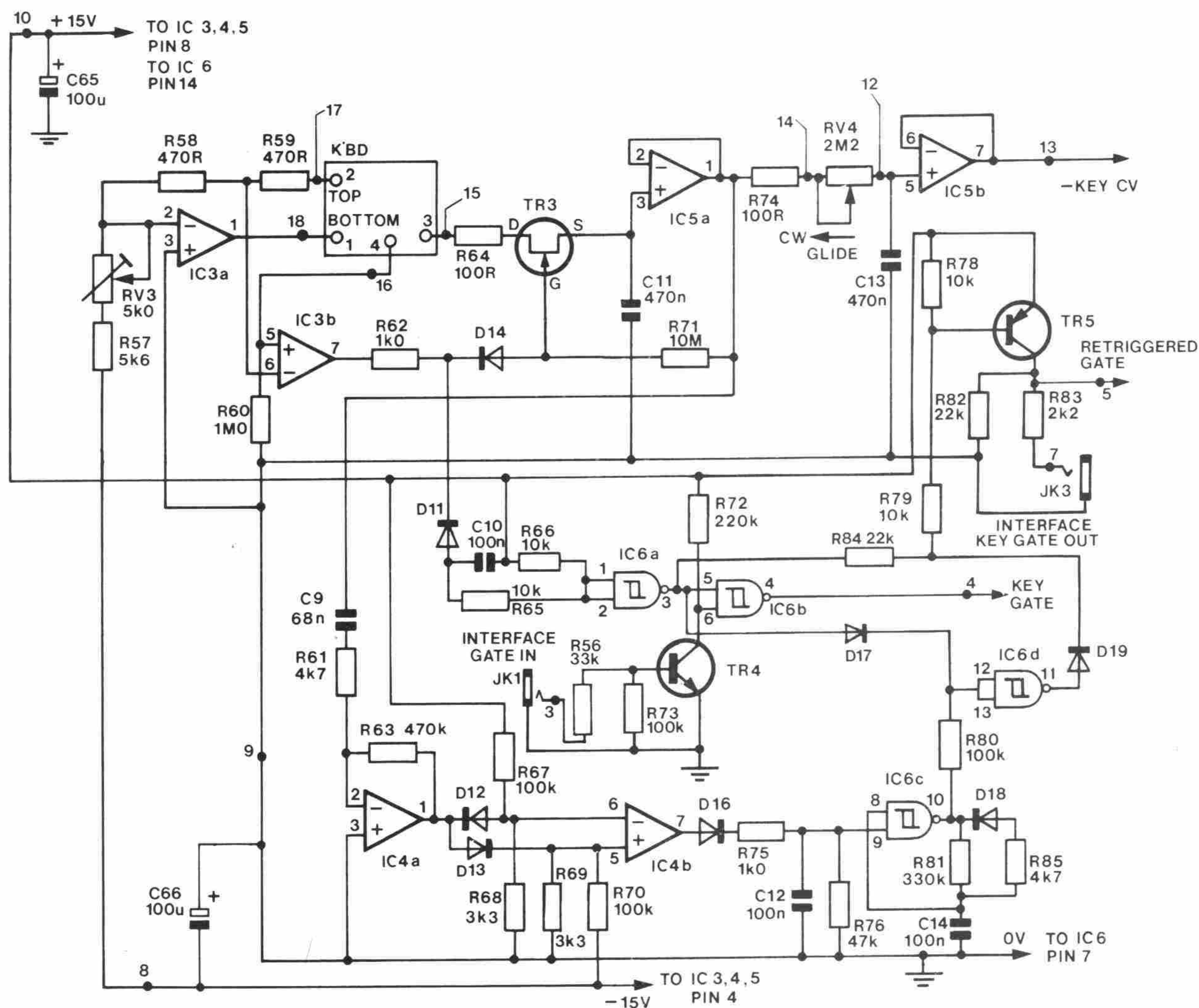

pulses from the LFO square wave to base 1 of TR7, the unijunction transistor in the rampwave generator. When the square wave goes low, the reset threshold of TR7 is effectively reduced by about 1 volt, so if the voltage on C15 is above +4V at this instant, the ramp wave is reset early and the sample-and-hold receives the voltage at the start of the next ramp cycle, i.e. -10V. The rampwave generator then runs normally until the next time it falls above +4V on a sample, whereupon it is reset and the sequence is repeated exactly. The time taken for this to occur depends upon the frequency ratio, but since the synchronisation is quite weak, sequences from very short to quite long are easily obtained and very long sequences are terminated when the premature reset condition arises.

VCOs and Associated Circuitry

Figure 9 shows the circuit diagram of the Voltage Controlled Oscillators. The oscillator control circuitry and the sections that combine the VCO signals by frequency modulation and synchronisation are also included.

Each VCO uses the CEM 3340 IC, which is specifically designed for this kind of application, allowing a versatile and precise VCO to be built with great improvements in cost, component count and specification over discrete designs. The CEM 3340 was fully

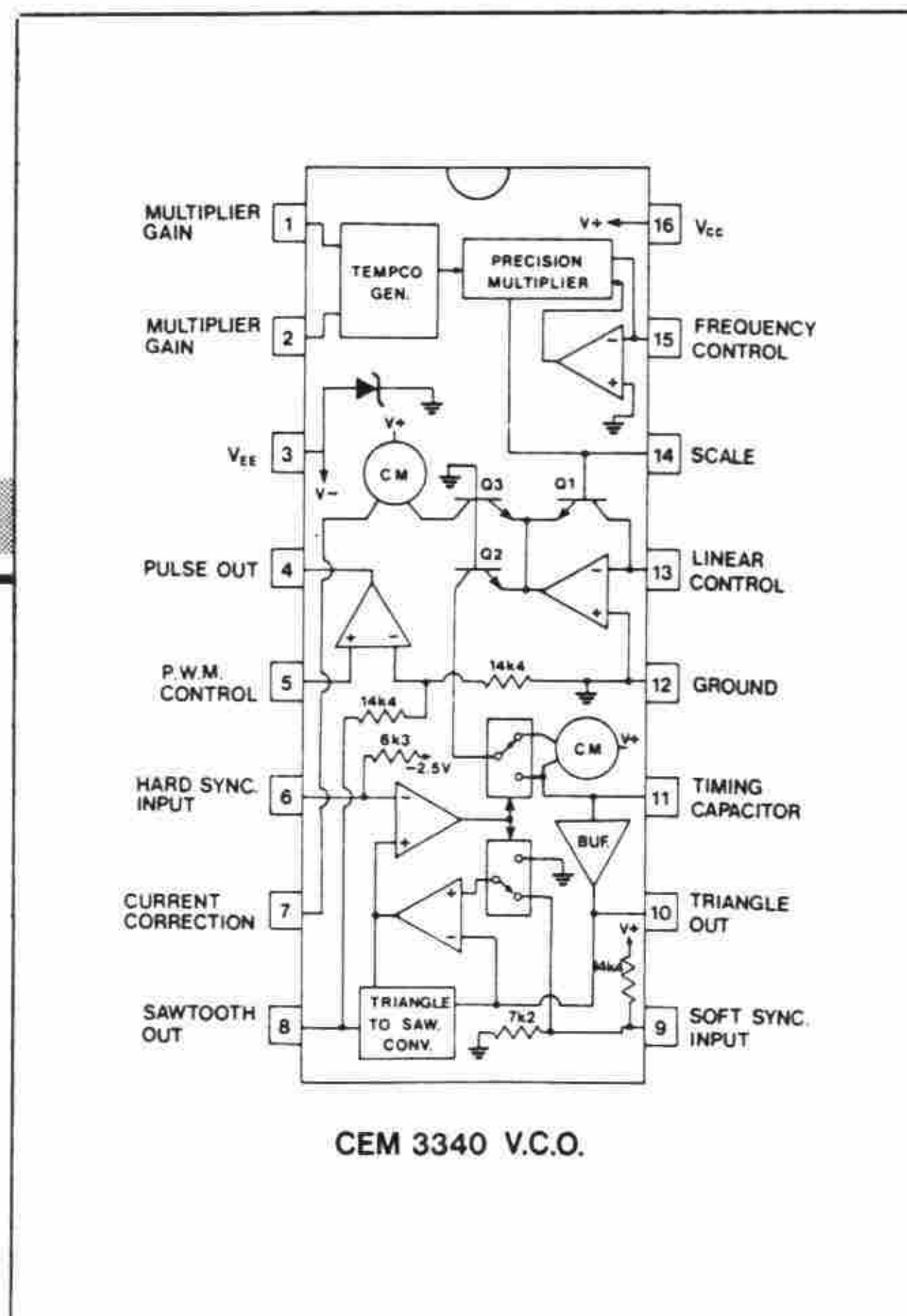


Figure 10. The CEM 3340.


described by Charles Blakey in 'IC's for Electromusic', E&MM March '81, so except where its usage in this design is unusual, we shall not discuss it in great depth here. The internal diagram is shown in Figure 10. The device is an exponential VCO with linear FM, sync, and pulse width control inputs. IC15 and IC16 are the basis of VCO 1 and VCO 2 respectively, and pin 15 of each is the exponential control input. This is a virtual earth summing node so each of the required signals for VCO pitch

control are routed to this point via a resistor whose value which determines the control relationship (the amount of pitch change for a given voltage change). With the scale trim presets correctly set, 100k gives the required keyboard control relationship of 1V/Octave.

IC7a inverts the output of the glide circuit, and applies an offset so that the middle 'C' of the keyboard generates a key CV of 0V. This simplifies interfacing with additional equipment. The 'Tune' pot. (RV5) shifts the pitch up to ± 2 semitones.

The key CV signal is fed to VCO1 and VCO2 via R162 and R163 respectively, which are 100k 1% metal film resistors with a temperature co-efficient of better than 100ppm/ $^{\circ}$ C. The precision is not important since the scale is trimmed, but the low temperature co-efficient is required to ensure that the control relationship remains constant with varying temperature. IC15 and IC16 are internally compensated for temperature changes, but stability of external

Figure 8. Low frequency oscillator circuit diagram.

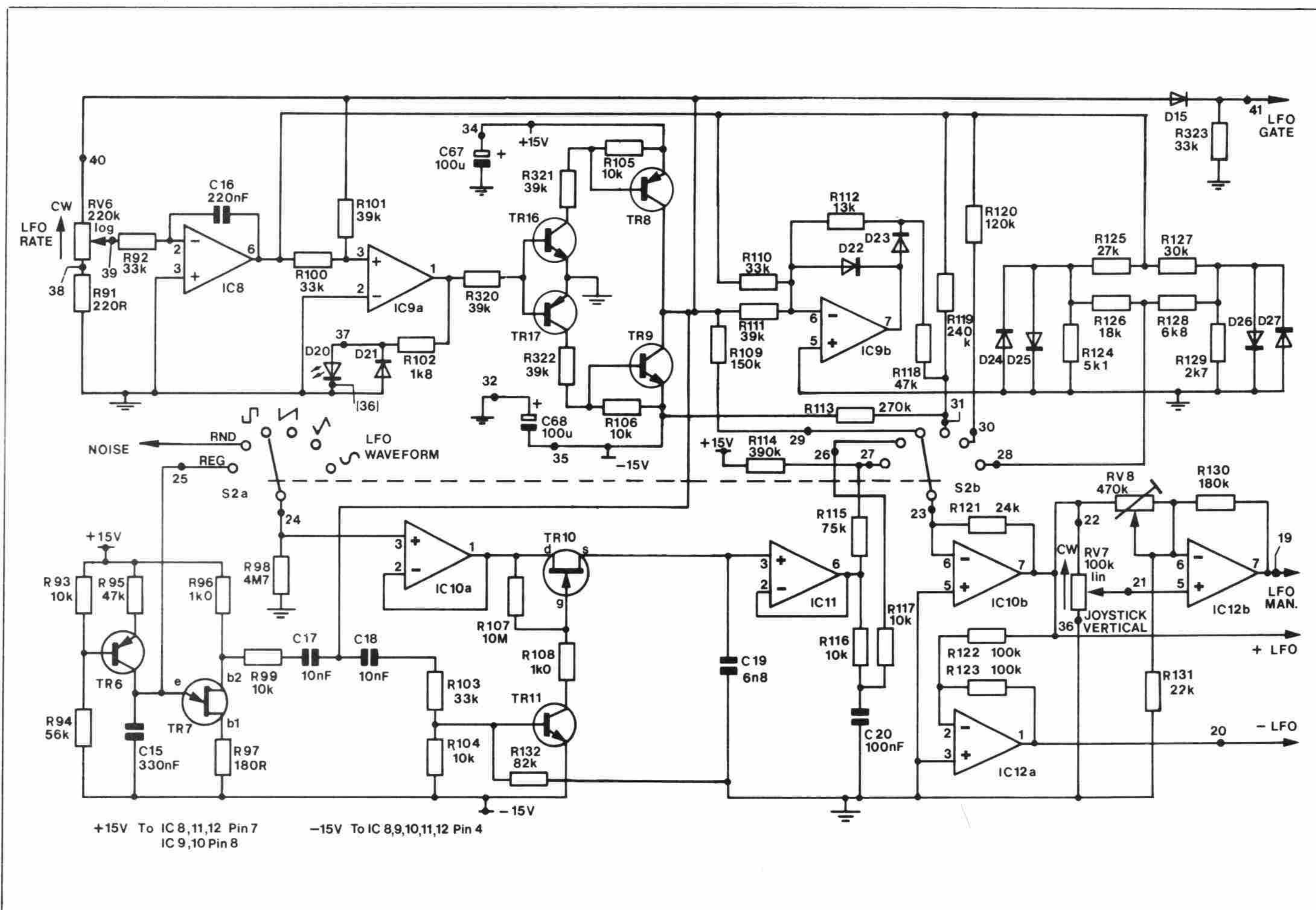



control signals is just as important where it affects control scale.

The VCO CV interface socket accepts an external voltage from a device such as a sequencer for additional precise control of the VCOs. The voltage is buffered by IC7b and fed to pin 15 of IC15 by R147, R164 and RV21, and to pin 15 of IC16 by R148, R165 and RV22. Though 100k 1% resistors would give a control scale as precise as that for the keyboard, the external CV must match key CV for scale exactly, so RV21 and RV22 are included. S5, RV15, S7, and R157-161 perform the Modulation routing for the VCOs.

The controller enables the joystick or an external device to control either or both oscillator pitches, pulse width, or filter cutoff frequency with variable depth. IC14a amplifies the voltage from the wiper of RV13, the x-axis joystick pot. With the controller in/out socket unused, RV14 controls the amount of joystick voltage modulating the function selected by S6.

Each VCO has a range selector switch which transposes the pitch up or down over a total range of six octaves. The voltages for the different ranges are provided by the potential divider composed of R133-R138, RV9-12 and RV19. The 64' position is connected to 0V, and so adds nothing to the basic pitch for each VCO set by RV17 and 18. Successively higher positions of the range switches S3 and S4 add 2.4 volts per position. R145 ensures the correct current/frequency relationship for VCO 1, while VCO 2's control input may be trimmed by RV20 so that the oscillators remain exactly in tune during octave switching.

The synchronisation circuit appears in the bottom right hand corner of Figure 9. S8b is the pole of the FM & Sync Function switch that controls this circuit. When sync is off (in the 'Off' and 'FM' positions) pin 13 of IC17d is held low blocking the pulse wave from VCO 1, the 'master' oscillator. When sync is selected, the pulse wave is inverted by the NAND gate and the falling edges are differentiated to give 10us wide negative pulses that turn TR15 on. TR16 and TR17 are FETs that provide a low resistance path from C34, the integrator capacitor of IC16, to the potential divider R215, RV29, RV30 when either gate is allowed to go high. Without sync selected, the FETs are held off by R212 via D29 and D30. With S8 in the 'Sync I' or 'FM + Sync I' position, the gate of

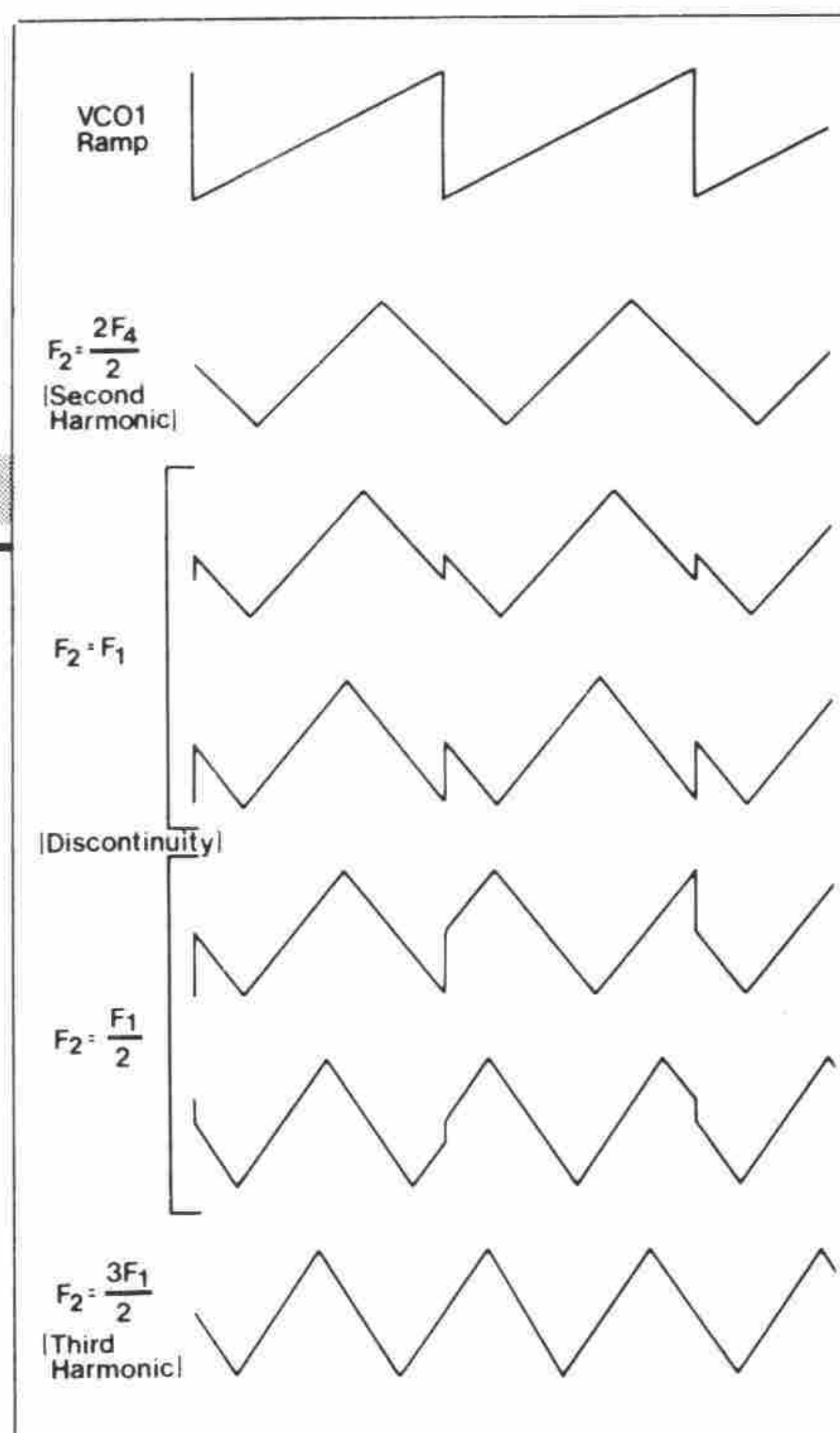


Figure 11. Sync. II.

TR17 is connected to -15V holding it off, but on each sync pulse R214 is allowed to turn on TR16, and C34 discharges to the voltage set by RV30. With Sync II selected TR16 is held off and TR17 discharges C34 to the voltage on the wiper of RV29. Hence, at the end of each cycle of VCO 1, VCO 2's waveform is reset to one of two positions depending on which type of synchronisation is selected.

The synchronisation control uses the pulse wave facility of the CEM 3340 to inhibit reset until the rampwave of VCO2 has passed a certain point in its cycle. Reference to Figure 10 shows that the pulse wave is normally derived from the rampwave by comparing it with the voltage at pin 5, the pulse width modulation input. The output at pin 4 is an open NPN emitter, which is high while the ramp waveform is below the PW control voltage. This output is connected to the junction of R210, R211 in the base circuit of TR15 so for the first portion of VCO2's cycle the TR15 is held off and the sync pulses are prevented from resetting the cycle. The proportion of the cycle for which sync reset is inhibited is determined by the setting of RV26, the synchronisation control, which supplies a variable voltage to the PW control input. With the


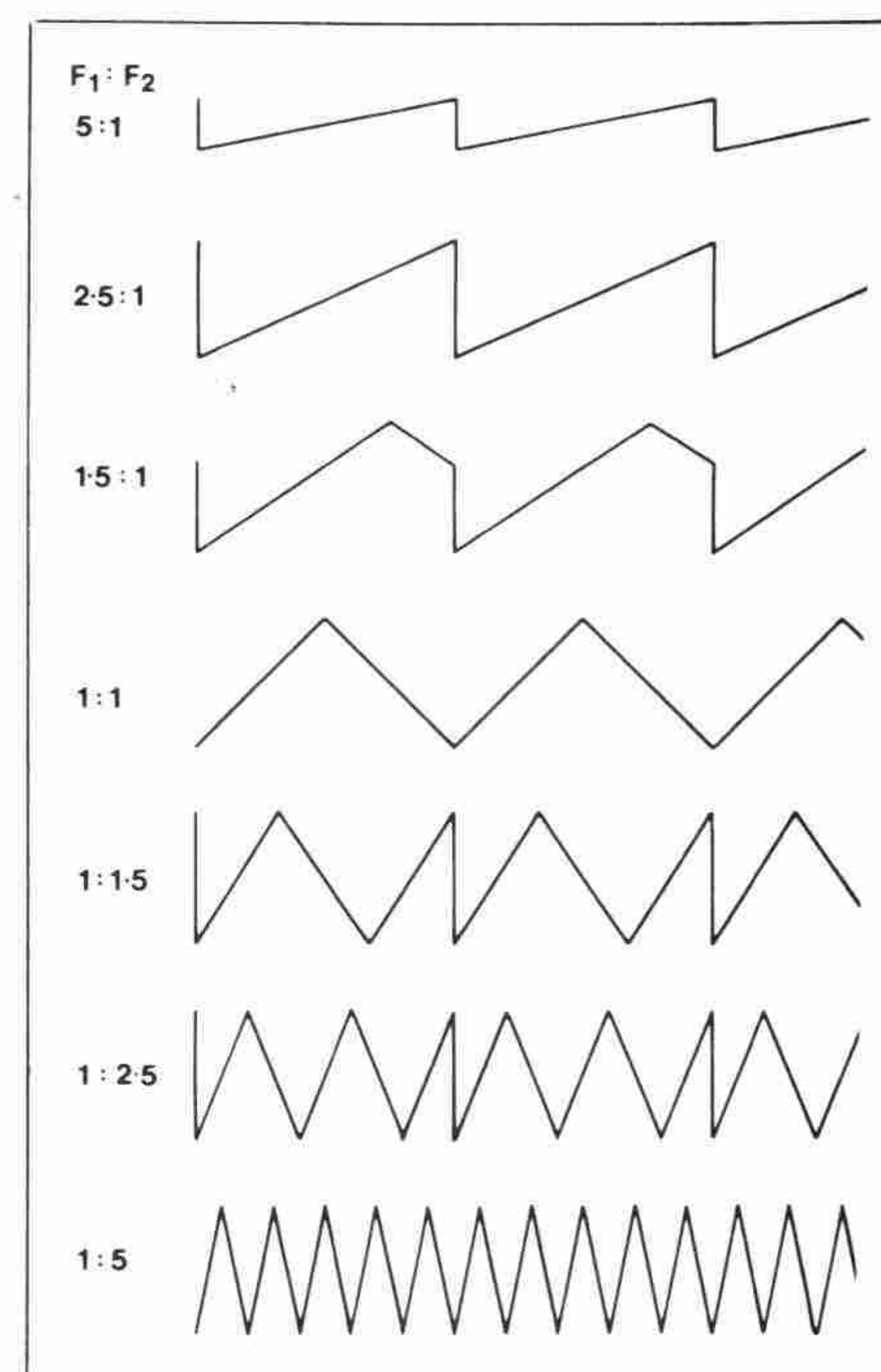


Figure 12. Sync. I.

synchronisation control at 0 (>5V at pin 5) no sync reset can occur. At 10 (0V at pin 5) the PW output at pin 4 has no effect and every sync pulse causes reset (hard sync).

When using soft synchronisation, the PW output of IC16 turns TR15 off as soon as the reset takes the ramp waveform below the voltage on the wiper of the sync control (the dotted line). This would cause the new cycle to begin at some point above 0V (or with Sync II above 2.5V) depending on the point it was at before the sync pulse. C38 is included to keep the FET on for a short time after the reset turns TR15 off, ensuring that C34 discharges to the voltage on the potential divider.

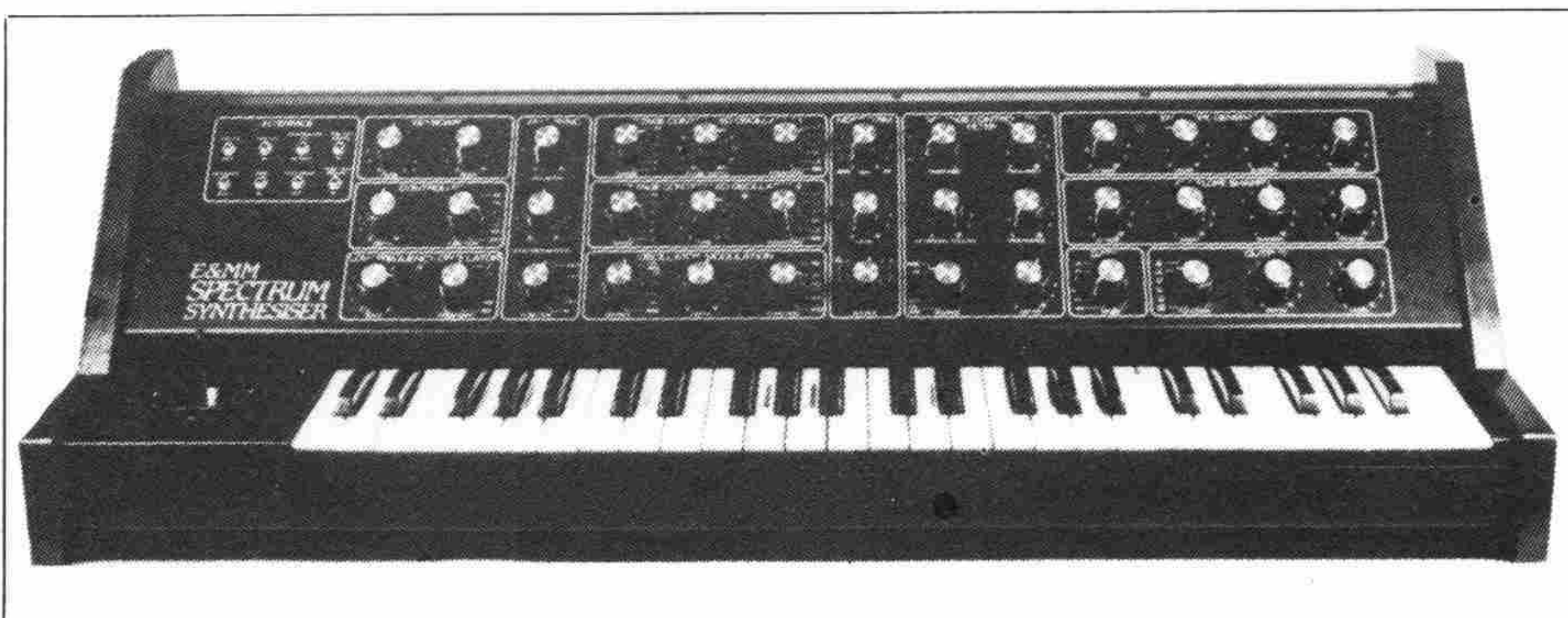The two sub-octave square waves are NAND-ed to provide the drive to the tuning LED. When the waveforms are out-of-phase, the output is high and the LED off. Advancing phase difference due to slightly different frequencies produces a pulse wave that varies from 100 to 50% width, displaying the beats as fluctuating LED brightness. **E&MM**



The SPECTRUM SYNTHESISER

Professional
Quality
Monophonic
Instrument

- ★ Low Cost
- ★ Easy to Construct
- ★ FM and Sync.
- ★ Stereo Outputs
- ★ Sequencer Effects
- ★ Interface Facilities
- ★ Four Octave Keyboard
- ★ Performance Controller

PART 2



PARTS COST
GUIDE
£200

Since publication of the Spectrum articles was delayed earlier this year, many improvements have been made to the original design. The synthesiser can still be built for around £200, plus cabinet, yet offers features found only on expensive commercial instruments.

For the benefit of newcomers to the magazine, and to bring our regular readers up to date with the improvements that have been made, we have

reprinted some of the original material. This is the final part of the project which contains sufficient information to enable experienced constructors to build the Spectrum. PCB track layouts and component overlays, cabinet drawings, a wiring chart and more comprehensive circuit descriptions are available in the Spectrum Synthesiser book, available from Maplin Publications for £1 plus 24p postage.

Ring Modulator and Noise

The ring modulator (Figure 15) is based around IC20 and processes the pulse wave of VCO1 and the triangle wave of VCO2 to produce complex non-harmonic sounds. It functions in a similar way to the rampwave shaper of the Spectrum LFO by inverting the triangle wave about its midpoint when the pulse wave is high, and leaving it unchanged when low. This constitutes four quadrant multiplication of the value of the triangle wave by the value of the pulse wave (-1 or +1). When the pulse output is low TR12 is off and the triangle wave is inverted with a gain of 2 by IC20a. The output is mixed with the original triangle wave of half the amplitude and opposite phase by IC20b. With the pulse output high the collector of TR12 is at -15V and the output of IC20a is positive. This reverse biases D32, and no signal reaches IC20b via R221. The original triangle wave is inverted by

IC20b and shifted by the current through R220. The output of IC20b is the required product.

The noise generator is quite conventional, using the thermal noise of a semiconductor junction as a source. TR14 amplifies the noise on the emitter of TR13 to about 4mV p-p, which is boosted to $\pm 2.5V$ by IC21. RV31 mixes the noise and RM signals, which are then fed to IC22, a transconductance amplifier which acts as a VCA. S11b selects the appropriate modulation source, which is conditioned by IC23. The LFO signals are symmetrical about 0V, whilst +EG swings from 0V to +5V and -EG goes from 0V to -5V. In order that all these signals have the same effect, therefore, an offset is selected by S11a and added to the modulation so that pin 6 of IC23 always swings between 0V (maximum gain) and about -14 volts. The CA3080 is really a current controlled amplifier, and so R237 converts this voltage swing into a control current. Since IC23 cannot completely cut this current off, R238

and diodes D33-D35 are included to ensure that the amplifier is truly off at the maximum negative control voltage.

The Filter


The heart of the filter is the CEM 3320 IC from Curtis Electromusic Specialities. Designed especially for use in voltage controlled filters, this IC contains four identical filter elements controlled by a temperature compensated exponential converter. Each element contains a transconductance type amplifier plus a buffer amplifier to avoid loading of the TCA's output. Depending on how the circuit is connected, either low pass or high pass filter sections may be created as in Figure 16; the three modes of the Spectrum's filter are formed by different combinations of these.

The low pass response is obtained with four low pass filter sections; since each section has a roll-off of -6dB/octave, the overall filter slope is -24dB/octave.


The band pass response has two low pass sections, preceded by two high pass sections so that only signals in a narrow range of frequencies are allowed through. The low band pass position, as you might expect, is a mixture of the preceding two configurations and consists of only one high pass section followed by three low pass stages. Switch S12 rearranges the signal paths and biasing around the IC to allow the three different configurations to be achieved.

IC24b is a four input mixer, accepting signals from the VCOs, the noise/RM VCA and the external input socket JK7. R242 is included to combat stray capacitance effects caused by the long leads to the VCO waveform selectors.

The CEM 3320 does not have a summing control input as the oscillators do, and so IC26 performs this function. As well as modulation inputs selected by S13, the key CV is fed in via the 'keyboard follow' control RV40. When this control is at maximum, the filter's cut-off frequency has the same 1V/octave law as the oscillators, and hence will track the keyboard so that the notes have a constant timbre. On most acoustic instruments, however, the upper notes have less harmonics than the lower ones, and if the key CV is attenuated by RV40 this effect may be obtained on the Spectrum. RV37 is included to allow setting up of the 1V/octave law, and if required, may be set to give the reverse of the above effect. In this case, setting the 'keyboard follow' control to 10 will cause higher notes to have more harmonics, and true keyboard following will occur at some lower setting.

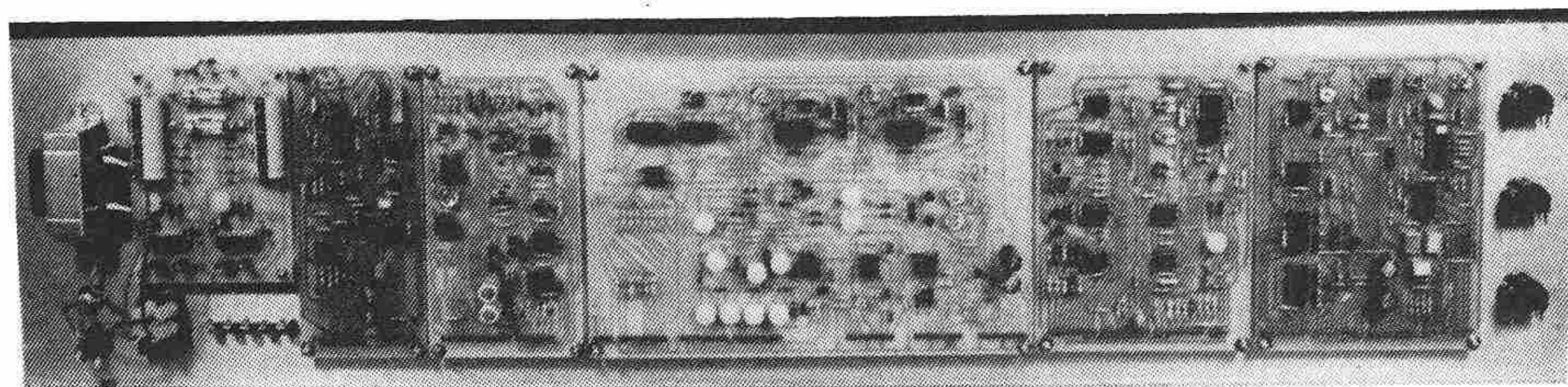

PCBs mounted on the back panel.

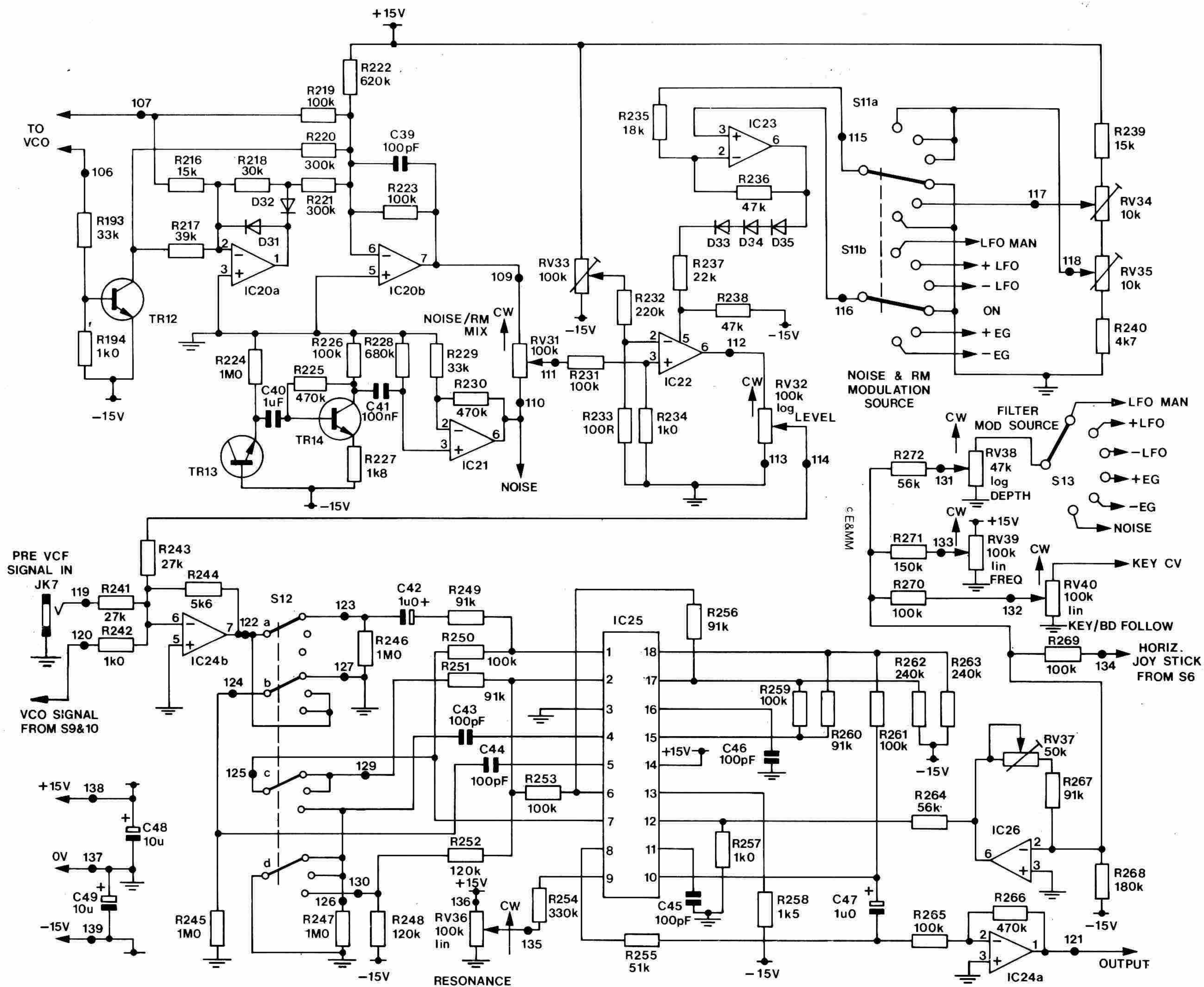

Voltage Controlled Amplifier and Pan

The last board in the synthesiser, but by no means the least, contains two VCAs and two envelope generators (EGs); the overall circuit is given in Figure 17. Both VCAs are contained in IC28, a CEM 3330.

IC28a performs the envelope shaping function, and is fed with the envelope signal via R274 since this IC works with current inputs and outputs rather than voltages. R273 performs the same function for the audio input, whilst IC29b converts the output current back into a voltage.

Panning and modulation are performed by IC28b, which works in an identical manner to IC28a; audio and control inputs are via R287 and R288 respectively, and output conversion is done by IC29c. When the FUNCTION switch S14 is in one of the MOD positions, both stereo outputs are connected to the second VCA, which then simply modulates the amplitude of the envelope shaper output according to the LFO waveform. IC30 amplifies and level shifts the selected waveforms so that the top end of RV42 always swings between 0 and +12V. Instead of going to 0V, which would cause IC28b to cut off the signal when the DEPTH control was at minimum, the other end of RV42 goes to a reference voltage generated by R292, 293, RV44 and buffered by IC27a.

In the pan mode, only one stereo output comes from the second VCA; the other is fed from the input of this VCA, the envelope shaper's output, via IC29d which subtracts the first channel's signal. This means that as one channel's output becomes louder, the other becomes softer and vice versa, in such a way that the total output is constant; so the volume is unaffected, but panning is achieved. The gain of the various circuits is arranged so that when IC28b is at around unity gain (100uA into pin 12) the output of the two channels is equal; i.e. 3V peak to peak with one VCO on, no filtering and RV45 at maximum. With full modulation, therefore, each output swings between zero and twice this figure.

IC29a combines half of each of the stereo outputs to give a mono signal of the same amplitude, which is affected by modulation but not by panning.

While the Spectrum's output is normally in the region of 3V pk-pk, 1V rms, factors such as modulation, resonance on the filter etc. can increase this to a maximum of 25V pk-pk. If required, the output may be attenuated by inserting resistors in series with the clockwise tags of RV45a and b. The output may be fed into any impedance greater than 25k; below about 10k, loss of bass may become apparent.

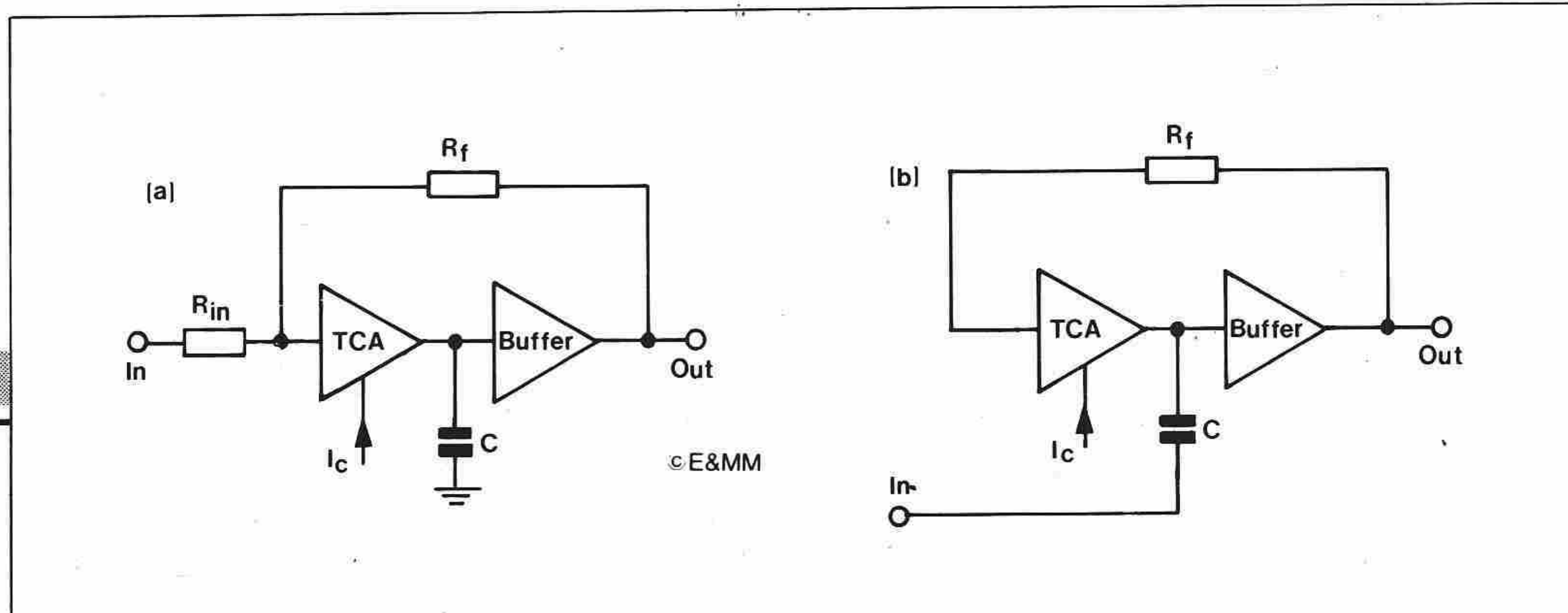


Figure 16. Single filter element of the CEM 3320. a) Low-pass. b) High-pass.

Envelope Generators

Once again, Curtis Electromusic come to the rescue and each envelope generator is built with a CEM 3310. Both circuits are identical in most respects, except that IC32 has an inverter on its output to provide EG+ and EG- signals, plus the circuitry for achieving key repeat.

R309 and 311, C59 and 61 set the speed range of each generator, and have been chosen to facilitate setting very fast attack times whilst allowing slow decay and release. These components affect all three times equally, and if desired, R309 and 311 may be increased to 'slow down' the envelope times.

Sustain level is controlled by RV48 and RV53. It is important that the sustain control voltage at pin 9 of each IC should not exceed the peak level attained during the attack phase; since this level is available on pin 3, the sustain pots are simply run from this voltage. If external modulation of sustain level was required, a more elaborate level sensing circuit would be necessary (as described in the Curtis data sheet).

Pin 4 is the gate input, and the trigger signal for pin 5 on each IC is derived by C57. In addition, IC33a and TR15 are brought into play on the 'repeat' and 'key repeat' functions; IC33a detects when the envelope output has reached the sustain level (i.e. the attack and decay phases are finished) and TR15 briefly pulls the trigger inputs high to restart both envelopes.

IC27b detects the signal at pin 16 of IC32, and lights D38 to indicate when this IC is in its attack phase.

Keyboard Construction

Use the printed circuit board as a template to mark the fixing holes on the

underside of the keyboard chassis. Mark them such that the edge of the board holding the bars will be about 5mm from the plungers and then drill for 6BA clearance. Fit the 48 divider resistors on the component side of the board along with the 12 veropins and solder in place. Cut the palladium bars to length and fit them to the track side using small loops of wire passed over the bar, through the mounting holes and twisted on the component side. Make sure each bar is well seated before soldering at each loop position on both sides.

The gate bar should lie flat on the PCB, whilst the S/H bar should be spaced away from the surface slightly by wrapping the mounting wire round the bar before soldering. This gives one wire diameter under the bar, and ensures more reliable contact.

Cut each plunger to length, leaving the nearest slot to the key end for the contact. Tin 5mm of both ends of the contact springs and fit each one by passing the thin end through the detached plunger and soldering it to the pad on the PCB. If you've marked the PCB mounting holes correctly then for proper operation the end of the spring should be about 2mm from the far edge of the pad. The positioning of the PCB and the springs on the PCB is not critical as long as when the PCB is mounted and the plungers clipped on, the springs are under slight tension to ensure positive contact. Mount the PCB to the chassis using 6BA bolts, 1/2" spacers and nuts, and washers to separate them further. The keys opposite the mounting positions will have to be temporarily removed to fit the bolts, and this should be done before drilling if a hand-held drill is used, to avoid the possibility of damage to the keys. Again, the spacing is not critical so long as all the contacts normally clear both bars and make contact with both when their keys are depressed. A 1/2" spacer and

one nut were found to be about right, though washers could be used if a high or low action to the keys is preferred. Connect the two halves of the board together using short wire links across the Veropin pairs. This completes the keyboard construction.

Setting Up

The power supply should be set up first; none of the other circuits will work without it, of course, and various voltages are derived from the + and -15 volt rails. Adjust the output voltages without the rest of the circuitry connected to begin with; RV1 sets the +15V output, RV2 the -15V. Use the most accurate voltmeter you can get hold of; a digital multimeter would be best, and an oscilloscope is likely to be more accurate than a cheap mechanical meter. On the prototype, the entire synthesiser consumed around 115mA on the +15V line, and 130mA on the -15V line. If you have a dual bench power supply, you may like to check the consumption of the rest of the synthesiser before connecting it to the PSU. If not, the Spectrum's supply has current limiting to protect it from faults, but it is still worthwhile to insert a current meter in each supply line in turn to check for excessive current drain. Once you are sure there is nothing drastically wrong, the power supply can be connected up to the rest of the circuitry. Connect the output socket(s) to an amplifier, and you should be able to persuade the synthesiser to make some sort of a noise, although it will probably be horribly out of tune. After allowing everything to warm up for as long as possible — 1 hour say — the rest of the circuits can be set up in the following order.

Keyboard Controller


Set the TUNE control to midpoint, and the GLIDE control to zero. Monitor the key CV output from the VCO (pin 99) with the most accurate voltmeter at your disposal. If the Spectrum is to be used with other equipment already calibrated at 1 volt per octave, a digital meter will be essential here; otherwise, this measurement is less critical.

Press middle C on the keyboard. The key CV should be roughly 0 volts; make a note of what it actually is. Now press the next C up from middle C, which should produce a key CV 1 volt above that for middle C. If it is more than this, turn RV3 clockwise and vice versa. The middle C key CV will now have changed, so repeat this procedure as many times as necessary to obtain the correct 1 volt per octave change.

VCO Octaves

The VCOs are the heart of the synthesiser, and time and trouble taken in setting them up carefully will be directly reflected in the final performance of the instrument. Some way of monitoring the oscillators' frequency and comparing it with a reference will be necessary. The ideal solution is a digital frequency meter, which combines monitor and reference in one.

Set VCO1's range to 8', and sound the first A up the keyboard; note its frequency, which will eventually be 220Hz; don't worry if it isn't.

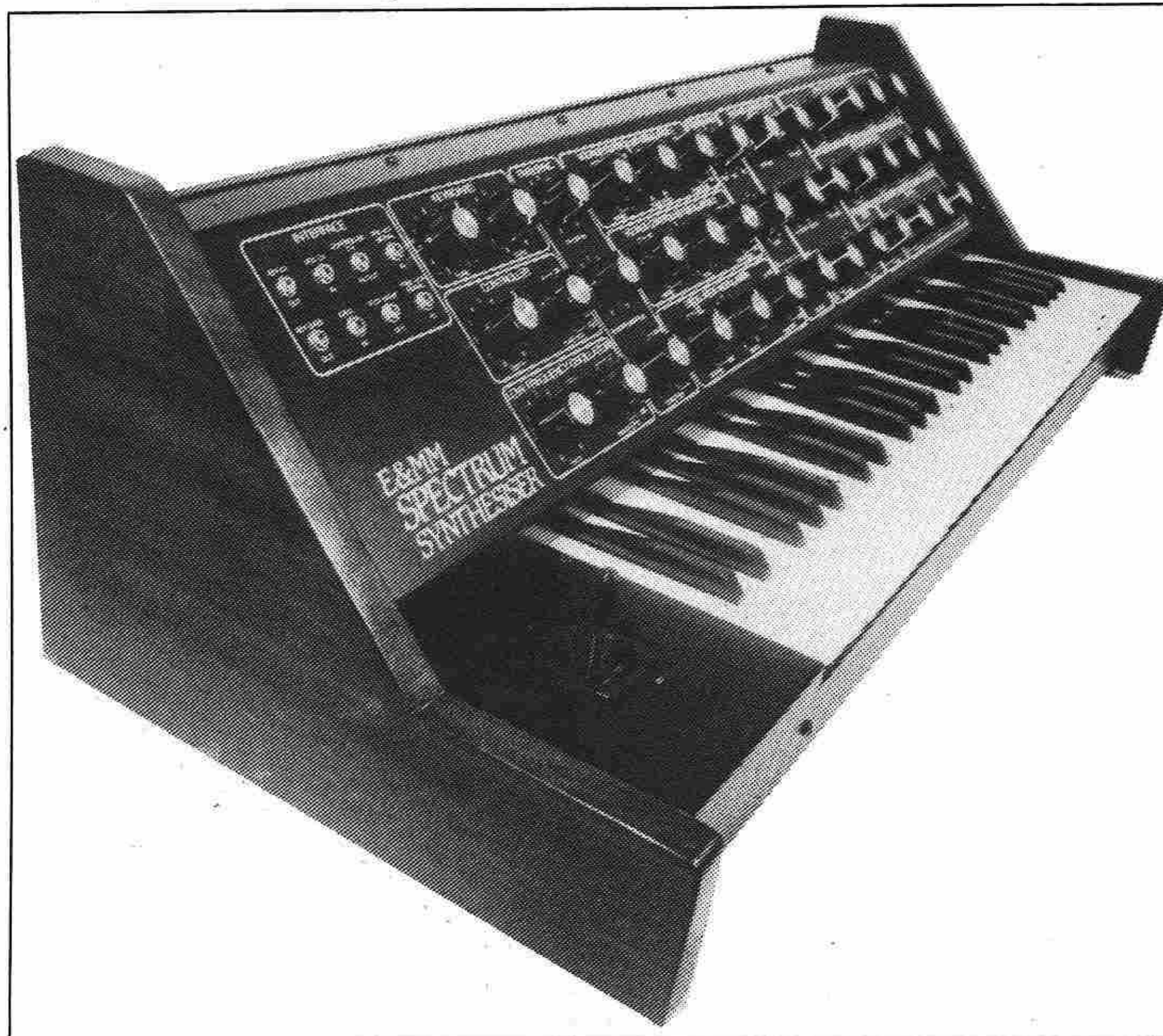


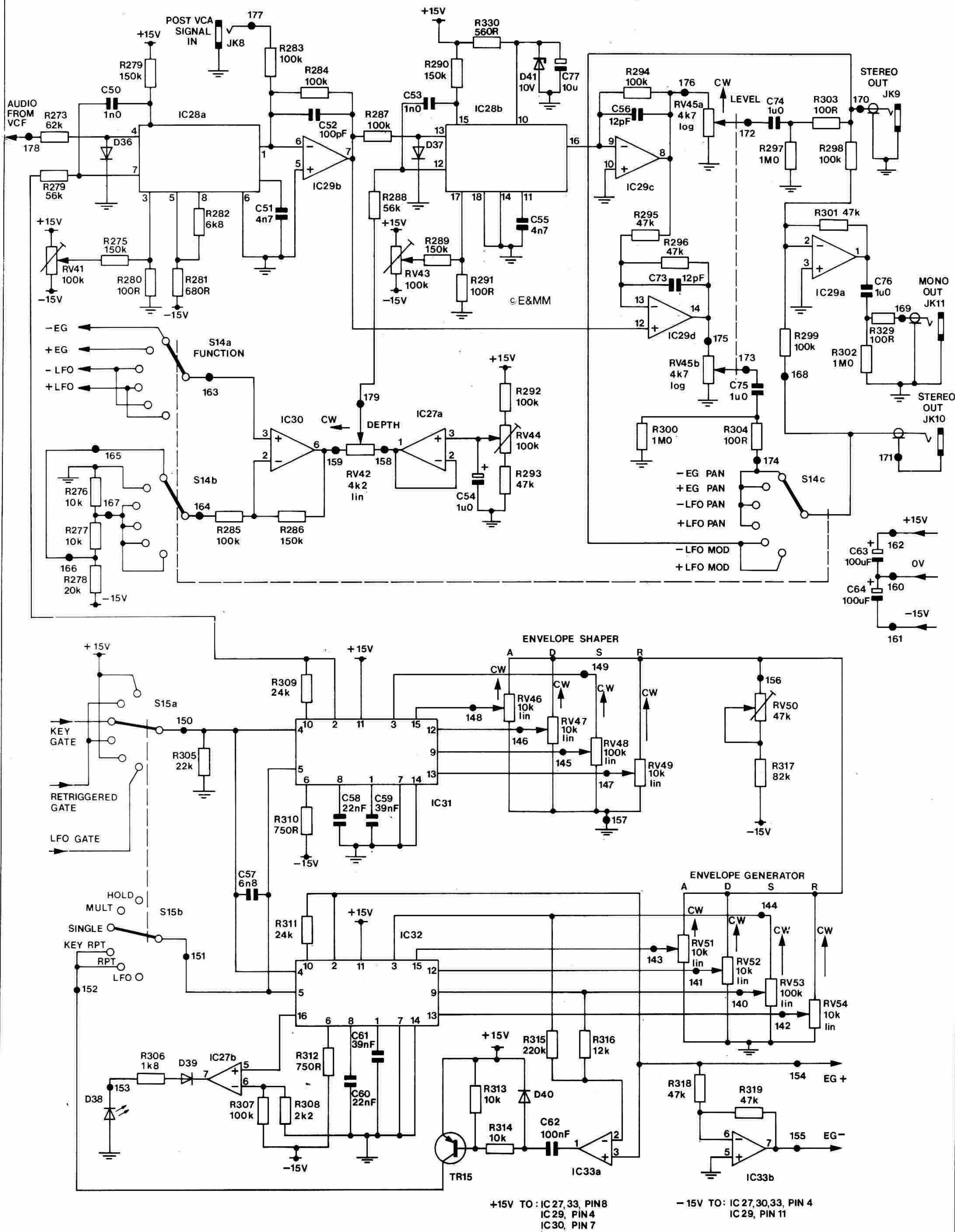


Figure 17. VCAs and envelope generators circuit diagram.

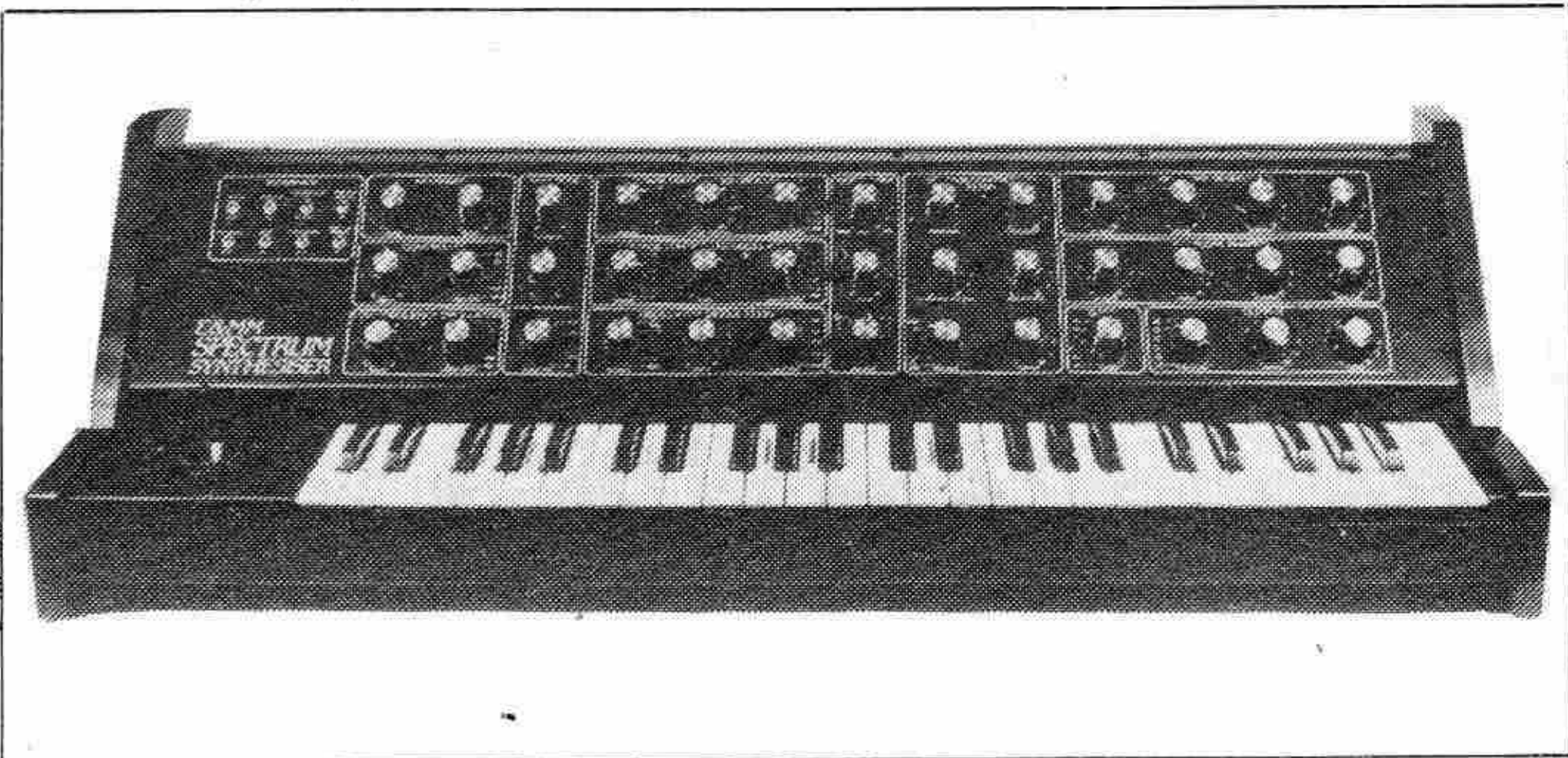

Press the second A up, and its frequency should be an octave above the first; i.e. exactly twice that of the first.

If it is flat, i.e. lower than it should be, turn RV23 anticlockwise and vice versa.

Now go back to the bottom A, which will also have changed, and repeat the process as many times as is necessary to obtain an exact doubling of frequency when going from the first A to the second.

The upper frequency range needs to be set separately; set VCO1's range to 2', and once again play two notes an octave apart. This time, leave RV23 strictly alone and adjust RV55 to give a doubling in frequency. The VCO will always be flat, so turn RV55 anticlockwise to correct this; this adjustment is not as critical as the basic low frequency one.

VCO2

No references are required for the rest of the tuning up; VCO2 is best adjusted with reference to VCO1 to ensure the two oscillators track exactly.

Listen to VCO1 and VCO2 together, both on the 8' range and with VCO2's TUNE control central. Press any note low on the keyboard, and tune the VCOs together with RV18. Now press a high note and, by switching VCO1 and VCO2 off alternately, determine whether VCO2 is sharp or flat in relation to VCO1. If it is flat, turn RV24 anticlockwise and vice versa.

Repeat the above paragraph until the oscillators stay in tune over the whole span of the keyboard, but without changing ranges at this point.

Now switch both VCOs to 2' range, and repeat the procedure, tuning RV56. VCO2 will always be flat to begin with, and so RV56 will need to be turned anticlockwise.

VCO Range Switches

Set both VCOs to the 64' range, play a high note, and tune the oscillators together using RV17 or 18. Switch VCO1 to 32' and adjust RV19 for minimum beating; then switch VCO2 to 32' and tune the VCOs together again with RV20. Switch VCO1 to 16' and adjust RV12, then switch VCO2 to 16' and both oscillators should be in tune; if not, trim RV20 very slightly. Switch VCO1 to 8' and adjust RV11; adjust RV10 with VCO1 on 4' and VCO2 on 8', and finally switch VCO1 to 2' and VCO2 to 4' and adjust RV9.

The oscillators should now remain in tune with each other over the whole range of the keyboard and range switches; in practice, slight anomalies in the control characteristics will prevent perfection being achieved, but only the slightest touch of VCO2 TUNE should be necessary to correct any mistracking.

VCOs — Final Adjustments

Once the oscillators are tracking satisfactorily, set VCO2 TUNE and the keyboard TUNE to mid position, and tune the second A up the keyboard to middle A, or 440Hz. RV17 tunes VCO1, and RV18 tunes VCO2. If the Spectrum is to be used with another instrument which cannot be tuned, you may prefer to tune up to that instead.

RV27 may be used to set the width of VCO2's pulse output, or simply left midway.

RV29 should be set to give 3.85 volts on its wiper, and RV30 to give 1.6 volts on its wiper.

The final VCO adjustment is to centre the horizontal joystick movement. Loosen RV13's clamp screw, shown in Figure 25. Set controller FUNCTION to VCO1, and DEPTH to 10, whereupon VCO1 will probably go wildly out of tune. Hold the joystick lever and RV13's trim tab central, and rotate the body of RV13 to bring VCO1 back into tune; then do up the clamp screw. Once the joystick is mounted, and after transporting the synthesiser, adjust the trim tab so that when the controller DEPTH control is rotated back and forth, no perceptible pitch change takes place.

LFO

RV8 is the only adjustment on the LFO. Set oscillator modulation as follows: SOURCE to LFO MAN, DEPTH to 10 and FUNCTION to VCO 1 + 2. Modulation of the VCOs will now be apparent; with the joystick lever and RV7's trim tab central, adjust RV8 until there is no modulation breakthrough.

Noise and RM VCA

Switch off both VCOs, and turn up the NOISE AND RM LEVEL. Select square wave output from the LFO, and turn noise & RM modulation SOURCE to +LFO. Turn RV35 fully anticlockwise, so that noise comes through loudly whilst the LFO LED is off, and quietly when it is on; a fairly slow LFO rate is advisable. Now turn RV35 clockwise until the noise is just cut off during the LED on periods. If any clicking or thumping is apparent as the LFO switches, adjust RV33 to get rid of it.

Now turn the SOURCE switch to +EG, turn the envelope generator SUSTAIN to zero, and turn RV34 fully anticlockwise. Some noise will now be heard on the Spectrum's output; turn RV34 clockwise until it just disappears. Turn down the noise LEVEL, and return SUSTAIN to 10.

Filter

RV37 adjusts the filter's volts per octave characteristic, which is not

nearly as critical (or difficult) as the adjustment of the VCOs, and may be done most simply by ear. Set the filter controls as follows: RESPONSE to BP, FREQUENCY about midway, KEYBOARD FOLLOW to 10, RESONANCE to 10 and DEPTH to 0. The filter should oscillate with a pure tone which can be played from the keyboard; to avoid confusion, make sure both VCOs and the noise & RM are off. Set RV37 midway, and play a scale on the keyboard; e.g. C major, all the white notes between one C and the next. If the scale sounds 'compressed' — as if it should go on longer to reach the proper note — turn RV37 clockwise, and vice versa.

Altering RV37 will also alter the tuning of the whole scale, but carry on playing and adjusting until the scale 'sounds right'; like the doh, re, mi... etc you learnt in school.

Finally turn the resonance down ready for the final setting up.

VCA and Pan

With the synthesiser still set to give no sound, turn the GATE MODE switch to LFO, set the envelope shaper SUSTAIN to 10 and ATTACK and RELEASE to 0. Turn up the LEVEL

control, and there will be a 'thump' each time the LFO switches (along with some background noise). Adjust RV41 to minimise this thump.

Now switch the GATE MODE back to HOLD, and select either LFO MOD on the OUTPUT FUNCTION selector; the LFO should still be giving a square wave. Turn up the DEPTH control, and the thumping will return, but sharper this time — more of a clicking sound. Adjust RV43 to get rid of this as far as possible. If necessary, keep turning up the amplifier's volume as these adjustments progress to keep the clicking audible.

Turn DEPTH back to minimum, select any 'pan' position on the FUNCTION switch, and monitor the stereo outputs with a dual beam 'scope or well-balanced amplifier and headphones. Turn on one of the VCOs, and adjust RV44 to give equal outputs from each channel.

Finally, adjust RV50 to give -0.24 volts on pin 156 — or the clockwise tag of any ATTACK, DECAY or RELEASE pot — with respect to 0V.

This completes the construction of the Spectrum Synthesiser. Articles on playing technique and details of a demonstration cassette will be published in future issues of E&MM.

KEYBOARD PARTS LIST

| | | | |
|---------------|-------------------------------|----------|---------|
| Resistors | | | |
| R8-55 | 47R 2% | 48 off | (X47R) |
| Miscellaneous | | | |
| | 49-note C-C keyboard | | (XB17T) |
| | Contact springs | 49 off | (QY07H) |
| | Palladium bars, 1.2mm x 330mm | Set of 4 | |
| | 24-contact PCB | | (GA09K) |
| | 25-contact PCB | | (GA10L) |
| | 6BA 1" bolts | | (BF67H) |
| | 6BA 1/2" spacers | | (FW35Q) |
| | 6BA washers | | (BF22Y) |
| | 6BA nuts | | (BF18U) |
| | Veropins | | (FL24B) |

POWER SUPPLY UNIT PARTS LIST

| | | | |
|---|-------------------------|--------|---------|
| Resistors — 5% 1/4W carbon unless specified | | | |
| R1,2 | 2R2 1/4W | 2 off | (S2R2) |
| R3,4 | 3k3 1% | 2 off | (T3K3) |
| R5,6 | 3k0 1% | 2 off | (T3K0) |
| R7 | 330R | | (M330R) |
| RV1,2 | 1k cermet preset | 2 off | (WR40T) |
| Capacitors | | | |
| C1,2 | 2200uF 25V axial elect. | 2 off | (FB90X) |
| C3,4,7,8 | 2u2 63V PC elect. | 4 off | (FF02C) |
| C5,6 | 100pF polystyrene | | (BX28F) |
| Semiconductors | | | |
| IC1,2 | uA723 14-pin DIL | 2 off | (QL21X) |
| TR1,2 | BD135 | 2 off | (QF06G) |
| D1-D10 | 1N4001 | 10 off | (QL73Q) |

| | | | |
|---------------|---------------------------------|-------|---------|
| Miscellaneous | | | |
| T1 | 240V prim. 0-15, 0-15 sec. 10VA | | (LY03D) |
| S1 | DPST rocker switch with neon | | (YR70M) |
| FS1 | 20mm 500mA quick blow fuse | | (WR02C) |
| | 20mm panel fuseholder | | (RX96E) |
| FS2,3 | 20mm 1A quick blow fuse | 2 off | (WR03D) |
| | 20mm chassis fuseholder | 2 off | (RX49D) |
| | 14-pin DIL socket | 2 off | (BL18U) |
| | PCB | | (GA03D) |
| | 3A 3-core mains cable 2m | | (XR01B) |
| | 13A mains plug | | (HL58N) |
| | 6BA 1" bolts | | (BF07H) |
| | 6BA 1/2" spacers | | (FW35Q) |
| | 6BA nuts | | (BF18U) |
| | 4BA 1/2" bolts | | (BF03D) |
| | 4BA nuts | | (BF17T) |
| | 4BA solder tags | | (BF28F) |
| | Cable grommet | | (LR48C) |
| | Veropins | | (FL24B) |

KEYBOARD CONTROLLER PARTS LIST

Resistors — 5% 1/3W carbon unless specified

| | | | |
|--------------|------------------------------|-------|---------|
| R56 | 33k | | (M33K) |
| R57 | 5k6 1% film | | (T5K6) |
| R58,59 | 470R 1% film | 2 off | (T470R) |
| R60 | 1M0 | | (M1M0) |
| R61,85 | 4k7 | 2 off | (M4K7) |
| R62,75 | 1k0 | 2 off | (M1K0) |
| R63 | 470k | | (M470K) |
| R64,74 | 100R | 2 off | (M100R) |
| R65,66,78,79 | 10k | 4 off | (M10K) |
| R67,70,73,80 | 100k | 4 off | (M100K) |
| R68,69 | 3k3 | 2 off | (M3K3) |
| R71 | 10M 10% | | (M10M) |
| R72 | 220k | | (M220K) |
| R76 | 47k | | (M47K) |
| R81 | 330k | | (M330K) |
| R82,84 | 22k | 2 off | (M22K) |
| R83 | 2k2 | | (M2K2) |
| RV3 | 5k0 multi-turn cermet preset | | (WR48C) |
| RV4 | 2M2 log. pot. | | (FW29G) |

Capacitors — polycarbonate unless specified

| | | | |
|-----------|---------------------|-------|---------|
| C9 | 68nF | | (WW39N) |
| C10,12,14 | 100nF | 3 off | (WW41U) |
| C11,13 | 470nF | 2 off | (WW49D) |
| C65,66 | 100uF 25V PC elect. | 2 off | (FF11M) |

Semiconductors

| | | | |
|------------------|----------|-------|---------|
| IC3,4 | 1458C | 2 off | (QH46A) |
| IC5 | CA3240E | | (WQ21X) |
| IC6 | CD4093BE | | (QW53H) |
| TR3 | 2N3819 | | (QR36P) |
| TR4 | BC182L | | (QB55K) |
| TR5 | BC212L | | (QB60Q) |
| D11-D19 (no D15) | 1N4148 | 8 off | (QL80B) |

Miscellaneous

| | | | |
|-------|-------------------|-------|---------|
| JK1,3 | 8 pin DIL socket | 3 off | (BL17T) |
| | 14 pin DIL socket | | (BL18U) |
| | 3.5mm jack socket | 2 off | (HF82D) |
| | PCB | | (GA55K) |
| | Veropins | | (FL24B) |

VCO PARTS LIST

Resistors — 5% 1/3W carbon unless specified

| | | | |
|-----------------|--------------|--------|---------|
| R77,89 | 27k 1% film | 2 off | (T27K) |
| R86,87,149 | | | |
| 150,176,178 | 1M0 1% film | 6 off | (T1M0) |
| R88 | 110k 1% film | | (T110K) |
| R90,143,210,211 | 10k | 4 off | (M10K) |
| R133 | 3k9 1% film | | (T3K9) |
| R134,135,136, | | | |
| 137 | 2k4 1% film | 4 off | (T2K4) |
| R138 | 3k0 1% film | | (T3K0) |
| R139 | 56k | | (M56K) |
| R140-142,144, | | | |
| 152-161,174, | | | |
| 180,187,188, | | | |
| 192,198-200, | | | |
| 205-207 | 100k | 25 off | (M100K) |
| R145 | 240k 1% film | | (T240K) |
| R146,166,167 | 220k 1% film | 3 off | (T220K) |
| R147,148 | 91k 1% film | 2 off | (T91K) |
| R151 | 2M2 10% | | (M2M2) |
| R162,163 | 100k 1% film | 2 off | (T100K) |
| R164,165 | 47k 1% film | 2 off | (T47K) |
| R168,171 | 24k 1% film | 2 off | (T24K) |
| R169,172 | 910R 1/2W | 2 off | (S910R) |

| | | | |
|-----------------|------------------------------|-------|---------|
| R170,175 | 510k 1% film | 2 off | (T510K) |
| R173 | 560k | | (M560K) |
| R177,179 | 5k6 1% film | 2 off | (T5K6) |
| R181,184,325, | | | |
| 327 | 470R | 4 off | (M470R) |
| R182,185 | 1k8 1% film | 2 off | (T1K8) |
| R183 | 300k 1/2W | | (S300K) |
| R186 | 180k | | (M180K) |
| R189 | 1k0 | | (M1K0) |
| R190 | 680k | | (M680K) |
| R191 | 120k | | (M120K) |
| R195,202 | 330k | 2 off | (M330K) |
| R196,203 | 240k 1/2W | 2 off | (S240K) |
| R197,204 | 150k | 2 off | (M150K) |
| R201,208 | 47k | 2 off | (M47K) |
| R209 | 3k3 | | (M3K3) |
| R212 | 68k | | (M68K) |
| R213,214 | 220k | 2 off | (M220K) |
| R215 | 6k8 | | (M6K8) |
| R324,326 | 1M0 | 2 off | (M1M0) |
| R328 | 100R | | (M100R) |
| RV9,10,11,12,19 | 1k0 cermet preset | 5 off | (WR40T) |
| RV14 | 10k log. pot. | | (FW22Y) |
| RV15 | 47k log. pot. | | (FW24B) |
| RV16,25 | 470k lin. pot. | 2 off | (FW07H) |
| RV17,18 | 100k cermet preset | 2 off | (WR44X) |
| RV20,21,22 | 50k cermet preset | 3 off | (WR43W) |
| RV23,24 | 10k multi-turn cermet preset | 2 off | (WR49D) |
| RV26 | 100k lin. pot. | | (FW05F) |
| RV27 | 100k min. horiz. preset | | (WR61R) |
| RV5,28 | 220k lin. pot. | 2 off | (FW06G) |
| RV29,30 | 2k2 min. horiz. preset | 2 off | (WR56L) |
| RV55,56 | 22k min. horiz. preset | 2 off | (WR59P) |

Capacitors — monolithic ceramic unless specified

| | | | |
|------------------|---------------------|-------|---------|
| C21,24,25,26,27, | | | |
| 28,29,30,33 | 100nF | 9 off | (YY11M) |
| C22,23 | 1nF | 2 off | (YY24B) |
| C31,34 | 1nF 1% polystyrene | 2 off | (BX56L) |
| C32,35,71,72 | 10nF | 4 off | (YY08J) |
| C36 | 1uF polycarb. | | (WW53H) |
| C37 | 270pF ceramic plate | | (WX61R) |
| C38 | 100pF polystyrene | | (BX28F) |
| C69,70 | 100uF 25V PC elect. | 2 off | (FF11M) |

Semiconductors

| | | | |
|-----------|----------------|-------|---------|
| IC7,14,19 | 1458C | 3 off | (QH46A) |
| IC13 | LF353 or TL082 | | (WQ31J) |
| IC15,16 | CEM 3340 | 2 off | |
| IC17 | CD4093BE | | (QW53H) |
| IC18 | CD4013BE | | (QX07H) |
| TR15 | BC212L | | (QB60Q) |
| TR16,17 | 2N3819 | 2 off | (QR36P) |
| D28 | Red LED | | (WL27E) |
| D29,30 | 1N4148 | 2 off | (QL80B) |

Miscellaneous

| | | | |
|-----------|----------------------------|-------|---------|
| S3-10 | Rotary switch 2-pole 6-way | 8 off | (FF74R) |
| RV7,13 | Joystick, 100k lin. pots. | | (XB09K) |
| JK2,4,5,6 | 3.5mm jack socket | 4 off | (HF82D) |
| | 8 pin DIL socket | 4 off | (BL17T) |
| | 14 pin DIL socket | 2 off | (BL18U) |
| | 16 pin DIL socket | 2 off | (BL19V) |
| | PCB | | (GA36P) |
| | Veropins | | (FL24B) |

FILTER BOARD PARTS LIST

Resistors — 5% 1/3W carbon unless specified

| | | | |
|---------------|-----------|--------|---------|
| R193,229 | 33k | 2 off | (M33K) |
| R194,242,257 | 1k0 | 3 off | (M1K0) |
| R216,239 | 15k | 2 off | (M15K) |
| R217 | 39k | | (M39K) |
| R218 | 30k 1/2W | | (S30K) |
| R219,223,226, | | | |
| 231,250,253, | | | |
| 259,261,265, | | | |
| 269,270 | 100k | 11 off | (M100K) |
| R220,221 | 300k 1/2W | 2 off | (S300K) |
| R222 | 620k 1/2W | | (S620K) |
| R224,245,246, | | | |
| 247 | 1M0 | 4 off | (M1M0) |
| R225,230,266 | 470k | 3 off | (M470K) |
| R227 | 1k8 | | (M1K8) |
| R228 | 680k | | (M680K) |
| R232 | 220k | | (M220K) |
| R233,234 | 100R | 2 off | (M100R) |
| R235 | 18k | | (M18K) |
| R236,238 | 47k | 2 off | (M47K) |
| R237 | 22k | | (M22K) |
| R240 | 4k7 | | (M4K7) |
| R241,243 | 27k | 2 off | (M27K) |
| R244 | 5k6 | | (M5K6) |

| | | | |
|--------------------------|-------------------------|-------|---------|
| R248,252 | 120k | 2 off | (M120K) |
| R249,251,256, 260,267 | 91k ½W | 5 off | (S91K) |
| R254 | 330k | | (M330K) |
| R255 | 51k ½W | | (S51K) |
| R258 | 1k5 | | (M1K5) |
| R262,263 | 240k ½W | 2 off | (S240K) |
| R264,272 | 56k | 2 off | (M56K) |
| R268 | 180k | | (M180K) |
| R271 | 150k | | (M150K) |
| RV31,36,39,40 | 100k lin. pot. | 4 off | (FW05F) |
| RV32 | 100k log. pot. | | (FW25C) |
| RV33 | 100k min. horiz. preset | | (WR61R) |
| RV34,35 | 10k min. horiz. preset | 2 off | (WR58N) |
| RV37 | 50k cermet preset | | (WR43W) |
| RV38 | 47k log. pot. | | (FW24B) |

Capacitors

| | | | |
|--------|--------------------|-------|---------|
| C39 | 100pF ceramic | | (WX56L) |
| C40 | 1uF polycarb. | | (WW53H) |
| C41 | 100nF polycarb. | | (WW41U) |
| C42,47 | 1u0 100V PC elect. | 2 off | (FF01B) |
| C43,46 | 100pF polystyrene | 4 off | (BX28F) |
| C48,49 | 10uF 35V PC elect. | 2 off | (FF04E) |

Semiconductors

| | | | |
|------------|----------------|-------|---------|
| IC20 | 1458C | | (QH46A) |
| IC21,23,26 | 741C | 3 off | (QL22Y) |
| IC22 | CA3080E | | (YH58N) |
| IC24 | LF353 or TL082 | | (WQ31J) |
| IC25 | CEM 3320 | | |
| TR12,13,14 | BC182L | 3 off | (QB55K) |
| D33,34,35 | 1N4148 | 3 off | (QL80B) |

Miscellaneous

| | | | |
|--------|----------------------------|-------|---------|
| S11,13 | Rotary switch 2-pole 6-way | 2 off | (FF74R) |
| S12 | Rotary switch 4-pole 3-way | | (FF76H) |
| JK7 | 3.5mm jack socket | | (HF82D) |
| | 8 pin DIL socket | 6 off | (BL17T) |
| | 18 pin DIL socket | | (HQ76H) |
| | PCB | | (GA57M) |
| | Veropins | | (FL24B) |

LFO PARTS LIST

Resistors — 5% ½W carbon unless specified

| | | | |
|--------------------------------|-------------------------|-------|---------|
| R91 | 220R | | (M220R) |
| R92,100,103, 110,323 | 33k | 5 off | (M33K) |
| R93,99,104,105, 106,116,117 | 10k | 7 off | (M10K) |
| R94 | 56k | | (M56K) |
| R95,118 | 47k | 2 off | (M47K) |
| R96,108 | 1k0 | 2 off | (M1K0) |
| R97 | 180R | | (M180R) |
| R98 | 4M7 10% | | (M4M7) |
| R101,111,320, 321,322 | 39k | 5 off | (M39K) |
| R108 | 1k8 | | (M1K8) |
| R107 | 10M 10% | | (M10M) |
| R109 | 150k | | (M150K) |
| R112 | 13k ½W | | (S13K) |
| R113 | 270k | | (M270K) |
| R114 | 390k | | (M390K) |
| R115 | 75k ½W | | (S75K) |
| R119 | 240k ½W | | (S240K) |
| R120 | 120k | | (M120K) |
| R121 | 24k ½W | | (S24K) |
| R122,123 | 100k | 2 off | (M100K) |
| R124 | 5k1 ½W | | (S5K1) |
| R125 | 27k | | (M27K) |
| R126 | 18k | | (M18K) |
| R127 | 30k ½W | | (S30K) |
| R128 | 6k8 | | (M6K8) |
| R129 | 2k7 | | (M2K7) |
| R130 | 180K | | (M180K) |
| R131 | 22k | | (M22K) |
| R132 | 82k | | (M82K) |
| RV6 | 220k log. pot. | | (FW26D) |
| RV8 | 470k min. horiz. preset | | (WR63T) |

Capacitors — polycarbonate unless specified

| | | | |
|-----|-------|--|---------|
| C15 | 330nF | | (WW47B) |
| C16 | 220nF | | (WW45Y) |

| | | | |
|--------|---------------------|-------|---------|
| C17,18 | 10nF | 2 off | (WW29G) |
| C19 | 6n8 | | (WW27E) |
| C20 | 100nF | | (WW41V) |
| C67,68 | 100uF 25V PC elect. | 2 off | (FF11M) |

Semiconductors

| | | | |
|------------|-------------------|-------|---------|
| IC8 | LF351 or TL081 | | (WQ30H) |
| IC9,10,12 | 1458 | 3 off | (QH46A) |
| IC11 | CA3140 (see text) | | (QH29G) |
| TR6,8,17 | BC212L | 3 off | (QB60Q) |
| TR7 | 2N2646 | | (QR14Q) |
| TR9,11,16 | BC182L | 3 off | (QB55K) |
| TR10 | 2N3819 | | (QR36P) |
| D20 | Red LED | | (WL27E) |
| D21-27,D15 | 1N4148 | 8 off | (QL80B) |

Miscellaneous

| | | | |
|----|----------------------------|--|---------|
| | PCB | | (GA53H) |
| | Veropins | | (FL24B) |
| S2 | Rotary switch 2-pole 6-way | | (FF74R) |

ENVELOPE SHAPER BOARD PARTS LIST

Resistors — 5% ½W carbon unless specified

| | | | |
|--|-------------------------|-------|---------|
| R273 | 62k ½W | | (S62K) |
| R274,288 | 56k | 2 off | (M56K) |
| R275,279,286, 289,290 | 150k | 5 off | (M150K) |
| R276,277,313, 314 | 10k | 4 off | (M10K) |
| R278 | 20k ½W | | (S20K) |
| R280,291,303, 304,329 | 100R | 5 off | (M100R) |
| R281 | 680R | | (M680R) |
| R282 | 6k8 | | (M6K8) |
| R283,284,285, 287,292,294, 298,299,307 | 100k | 9 off | (M100K) |
| R293,295,296, 301,318,319 | 47k | 6 off | (M47K) |
| R297,300,302 | 1M | 3 off | (M1M0) |
| R305 | 22k | | (M22K) |
| R306 | 1k8 | | (M1K8) |
| R308 | 2k2 | | (M2K2) |
| R309,311 | 24k ½W | 2 off | (S24K) |
| R310,312 | 750R ½W | 2 off | (S750R) |
| R315 | 220k | | (M220K) |
| R316 | 12k | | (M12K) |
| R317 | 82k | | (M82K) |
| R330 | 560R | | (M560R) |
| RV41,43,44 | 100k min. horiz. preset | 3 off | (WR61R) |
| RV42 | 4k7 lin. pot. | | (FW01B) |
| RV45 | 4k7 log. dual gang pot. | | (FX08J) |
| RV46,47,49,51, 52,54 | 10k lin. pot. | 6 off | (FW02C) |
| RV48,53 | 100k lin. pot. | 2 off | (FW05F) |
| RV50 | 47k min. horiz. preset | | (WR60Q) |

Capacitors — polycarbonate unless specified

| | | | |
|-----------|---------------------|-------|---------|
| C50,53 | 1nF ceramic plate | 2 off | (WX68Y) |
| C51,55 | 4n7 | 2 off | (WW26D) |
| C52 | 100pF ceramic plate | | (WX56L) |
| C54 | 1u0 100V PC elect. | | (FF01B) |
| C56,73 | 12pF ceramic plate | 2 off | (WX46A) |
| C57 | 6n8 | | (WW27E) |
| C58,60 | 22nF | 2 off | (WW33L) |
| C59,61 | 39nF | 2 off | (WW36P) |
| C62 | 100nF | | (WW41U) |
| C63,64 | 100uF 25V PC elect. | 2 off | (FF11M) |
| C74,75,76 | 1u0 | 3 off | (WW53H) |
| C77 | 10u 35V PC elect. | | (FF04E) |

Semiconductors

| | | | |
|--------------|-----------------|-------|---------|
| IC27,33 | 1458C | 2 off | (QH46A) |
| IC28 | CEM 3330 | | |
| IC29 | LF347 | | (WQ29G) |
| IC30 | 741C | | (QL22Y) |
| IC31,32 | CEM 3310 | 2 off | |
| TR15 | BC212L | | (QB60Q) |
| D36,37,39,40 | 1N4148 | 4 off | (QL80B) |
| D38 | Red LED | | (WL27E) |
| D41 | 10V 400mW zener | | (QH14Q) |

Miscellaneous

| | | | |
|-----------|--|-------|---------|
| S14 | Shaft assembly and 2-pole 6-way wafer | 2 off | (FH46A) |
| | Rotary switch 2-pole 6-way | | (FF74R) |
| S15 | 3.5mm jack socket | | (HF82D) |
| JK8 | Standard mono jack socket | 3 off | (BW78K) |
| JK9,10,11 | 8 pin DIL socket | 3 off | (BL17T) |
| | 14 pin DIL socket | | (BL18U) |
| | 16 pin DIL socket | 2 off | (BL19V) |
| | 18 pin DIL socket | | (HQ76H) |
| | PCB | | (GA59P) |

The CEM ICs are only available from Digisound Ltd, 13 The Brooklands, Wrea Green, Preston, Lancs PR4 2NQ. The price for the set of 6 is £32.43 inc. VAT, p&p. The remainder of the parts, including a drilled joystick mounting plate and front panel finished in black with white legend, may be obtained from Maplin Electronic Supplies Ltd, PO Box 3, Rayleigh, Essex SS6 8LR; Order number LW60Q, price £167.50 inc. VAT and U.K. inland carriage. The front panel and joystick panel are available separately; order nos. are XG08J (£14.95 + £7 UK car.) & XX46A (£1.80) respectively.

Drilled joystick black mounting plate.
Drilled black front panel with white legend.